
TE 364: Communication Circuits

Lecture 8

Filter Circuits 2

2015.02.15

Abdul-Rahman Ahmed

Insertion-Loss Method

- Provides ways to shape pass- and stop-bands of the filter,
 - ❖ although its design theory is much more complex
- Power Loss Ratio, P_{LR}

$$P_{LR} = \frac{\text{power incident at port 1}}{\text{power delivered to the load connected at port 2}} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

- ❖ Expressed in decibel, it is called the *insertion loss*

Insertion-Loss Method

$$\Gamma(\omega^2) = \frac{f_1(\omega^2)}{f_1(\omega^2) + f_2(\omega^2)}$$

$$P_{LR} = 1 + \frac{f_1(\omega^2)}{f_2(\omega^2)}$$

$f_1(\omega^2)$ and $f_2(\omega^2)$ are real polynomials of ω^2

Insertion-loss Method

□ Magnitude of the voltage gain of the 2-port is

$$|G(\omega)| = \frac{1}{\sqrt{P_{LR}}} = \frac{1}{\sqrt{1 + f_1(\omega^2)/f_2(\omega^2)}}$$

□ Design Procedure

- ❖ Begin with lumped-element low-pass prototype
 - Synthesized from normalized tables
- ❖ Low-pass then transformed to required cut-off and impedance.
- ❖ Prototype transformed to high-pass, band-pass etc.
- ❖ Lumped elements then transformed to t-lines

Maximally Flat Filter

- ❑ Flattest possible pass-band response
- ❑ Also known as
 - ❖ Butterworth filter
 - ❖ Binomial filter

$$|G(\omega)| = \frac{1}{\sqrt{1 + \zeta \omega^{2n}}}$$

n is the order of the filter


ζ controls the power-loss ratio at its band edge

ω is the normalized frequency

Maximally Flat Filter

□ Insertion loss is given by
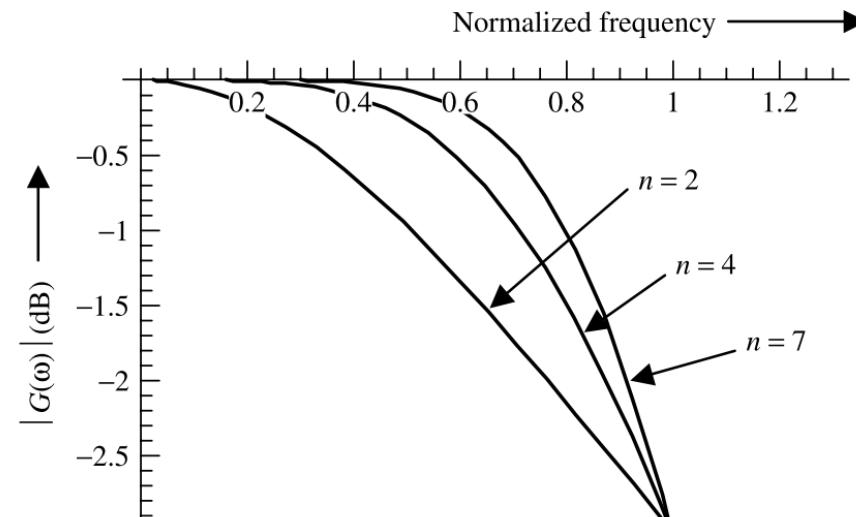
$$L = -20 \log_{10} \frac{1}{\sqrt{1 + \zeta \left(\frac{\omega}{\omega_c} \right)^{2n}}} = 10 \log_{10} \left[1 + \zeta \left(\frac{\omega}{\omega_c} \right)^{2n} \right]$$



Maximally Flat Filter

□ At the band edge,

$$\omega = \omega_c$$

and

$$\zeta = 10^{L_c/10} - 1$$

□ The order n can be obtained from

$$n = \frac{1}{2} \times \frac{\log_{10}(10^{L/10} - 1) - \log_{10} \zeta}{\log_{10}(\omega/\omega_c)}$$

Chebyshev Filter

- ❑ For Chebyshev Filters,
 - ❖ Flat pass-band is sacrificed for sharper cut-off
- ❑ Therefore
 - ❖ Possess ripples in the pass-band
 - ❖ Have sharp transition into the stop-band
- ❑ Chebyshev polynomials are used
 - ❖ To represent the insertion loss

Chebyshev Filter

□ Mathematically,

$$|G(\omega)| = \frac{1}{\sqrt{1 + \zeta T_m^2(\bar{\omega})}} \quad m = 1, 2, 3, \dots$$

T_m is a Chebyshev polynomial

ζ is a constant that controls the power-loss ratio at its band edge

$\bar{\omega}$ is the normalized frequency

Chebyshev Filter

□ The insertion loss is given by

$$L = -20 \log_{10} \frac{1}{\sqrt{1 + \zeta T_m^2(\omega/\omega_c)}} \\ = 10 \log_{10} \left[1 + \zeta T_m^2 \left(\frac{\omega}{\omega_c} \right) \right]$$

❖ Or

Chebyshev Filter

$$L = \begin{cases} 10 \log_{10} \left[1 + \zeta \cos^2 \left(m \cos^{-1} \frac{\omega}{\omega_c} \right) \right] & 0 \leq \omega \leq \omega_c \\ 10 \log_{10} \left[1 + \zeta \cosh^2 \left(m \cosh^{-1} \frac{\omega}{\omega_c} \right) \right] & \omega_c < \omega \end{cases}$$

□ Where

$$\zeta = 10^{0.1 \times G_r} - 1$$

□ G_r is the ripple amplitude in decibel


Chebyshev Filter

$$m = \frac{\cosh^{-1} \sqrt{(10^{0.1 \times L} - 1) / (10^{0.1 \times G_r} - 1)}}{\cosh^{-1} (\omega / \omega_c)}$$

□ Where

❖ L is the required insertion loss at frequency ω

Chebyshev Filter

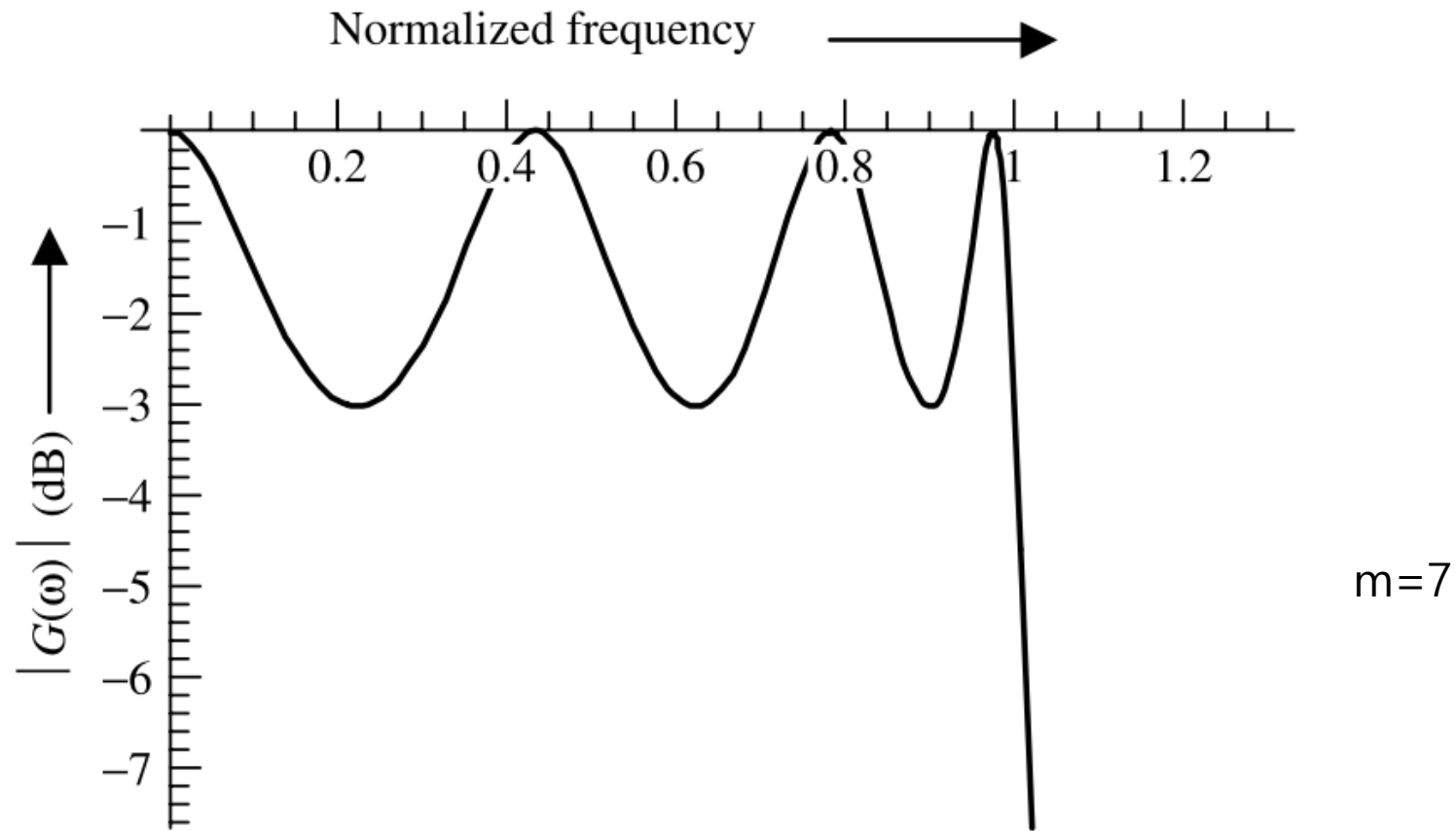

Chebyshev Filter

❖ *Example*

- It is desired to design a maximally flat low-pass filter with at least 15 dB attenuation at $\omega = 1.3\omega_c$ and -3 dB at its band edge. How many elements will be required for this filter? If a Chebyshev filter is used with a 3-dB ripple in its pass-band, find the number of circuit elements.

❖ *Solution*

$$\zeta = 10^{0.1 \times L_c} - 1 = 10^{0.3} - 1 = 1$$

$$n = \frac{1}{2} \times \frac{\log_{10}(10^{L/10} - 1) - \log_{10} \zeta}{\log_{10}(\omega/\omega_c)} = 0.5 \times \frac{\log_{10}(10^{1.5} - 1)}{\log_{10}(1.3)} = 6.52$$

Therefore, seven elements will be needed for this maximally flat filter.

Chebyshev Filter


❖ In the case of Chebyshev filter

$$m = \frac{\cosh^{-1} \sqrt{(10^{0.1 \times L} - 1) / (10^{0.1 \times G_r} - 1)}}{\cosh^{-1}(\omega / \omega_c)} = \frac{\cosh^{-1} \sqrt{(10^{1.5} - 1)}}{\cosh^{-1}(1.3)} = 3.17$$

❖ Therefore, only 3 elements are required

Low-Pass Filter Synthesis

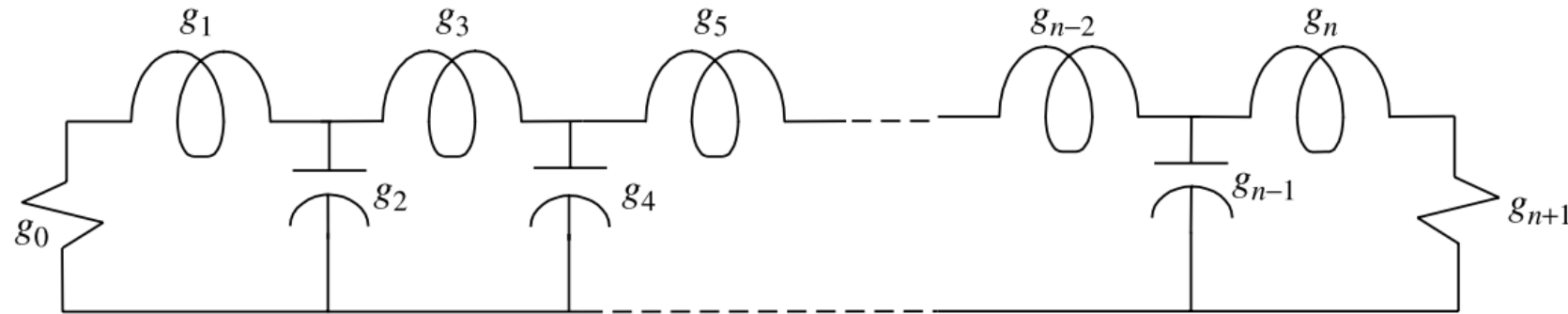□ Doubly terminated low-pass ladder network



- ❖ g signifies the roots of an n th-order transfer function that govern the characteristics of the filter.
- ❖ These represent the normalized reactance values of filter elements with a cut-off frequency $\omega_c = 1$.

□ The source resistance is represented by g_0 , and load is g_{n+1} .

Low-Pass Filter Synthesis

- The filter is made up of
 - ❖ series inductors and shunt capacitors that are in the form of cascaded T-networks.
- Another possible configuration is
 - ❖ a cascaded π -network that is obtained after replacing g_1 by a short circuit,
 - ❖ connecting a capacitor across the load g_{n+1} , and
 - ❖ renumbering the filter elements 1 through n .
- Elements are determined from the n roots of transfer function.

Low-Pass Filter Synthesis

- ❑ The transfer function is selected according to the pass- and stop-band characteristics desired.
- ❑ Normalized values of elements are then found from the roots of that transfer function.
- ❑ These values are then adjusted according to
 - ❖ the desired cut-off frequency and
 - ❖ the source and load resistance.

Summary of Design Procedure for Maximally Flat LP Filters

□ Assume that the cut-off frequency is given as $\omega_c = 1$

□ For Butterworth

❖ $g_0 = g_{n+1} = 1$

❖ $g_p = 2 \sin \frac{(2p-1)\pi}{2n} \quad p = 1, 2, 3, \dots$

❖ Such element values are given in the following table

Summary of Design Procedure for Maximally Flat LP Filters

□ Design values for Low-pass Binomial Filter Prototype

TABLE 9.4 Element Values for Low-Pass Binomial Filter Prototypes ($g_0 = 1$, $\omega_c = 1$)

n	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8
1	2.0000	1.0000						
2	1.4142	1.4142	1					
3	1.0000	2.0000	1.0000	1.0000				
4	0.7654	1.8478	1.8478	0.7654	1.0000			
5	0.6180	1.6180	2.0000	1.6180	0.6180	1		
6	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	1	
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.445	1.0000

Summary of Design Procedure for Chebyshev LP Filters

$$g_0 = 1$$

$$g_{m+1} = \begin{cases} 1 & m \text{ is an odd number} \\ \coth \frac{\xi}{4} & m \text{ is even number} \end{cases}$$

$$g_1 = \frac{2a_1}{\chi}, \text{ and}$$

$$g_p = \frac{4a_{(p-1)}a_p}{b_{(p-1)}g_{(p-1)}} \quad p = 1, 2, \dots, m$$

$$\xi = \ln \left(\coth \frac{G_r}{17.37} \right)$$

$$\chi = \sinh \frac{\xi}{2m}$$

$$a_p = \sin \frac{(2p-1)\pi}{2m}$$

$$b_p = \chi^2 + \sin^2 \frac{p\pi}{m}$$

Summary of Design Procedure for Chebyshev LP Filters

□ Design values for Low-pass Binomial Filter Prototype

TABLE 9.5 Element Values for Low-Pass Chebyshev Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, and 0.1 dB ripple)

m	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8
1	0.3053	1.000						
2	0.8431	0.6220	1.3554					
3	1.0316	1.1474	1.0316	1.0000				
4	1.1088	1.3062	1.7704	0.8181	1.3554			
5	1.1468	1.3712	1.9750	1.3712	1.1468	1.0000		
6	1.1681	1.4040	2.0562	1.5171	1.9029	0.8618	1.3554	
7	1.1812	1.4228	2.0967	1.5734	2.0967	1.4228	1.1812	1.0000

Scaling the Prototype to the Desired Cutoff Frequency and Load

- ❑ Frequency scaling from 1 to ω_c .
 - ❖ divide all normalized g values that represent capacitors or inductors by the desired cut-off frequency expressed in radians per second.
 - ❖ Resistors are excluded from this operation.
- ❑ Impedance scaling g_0 and g_{n+1} to $X \Omega$ from unity.
 - ❖ multiply all g values that represent resistors or inductors by X .
 - ❖ On other hand, divide those g values representing capacitors by X .

LP Butterworth example

❖ *Example*

- Design a Butterworth filter with a cut-off frequency of 10 MHz and an insertion loss of 30 dB at 40 MHz. It is to be used between a 50 Ω load and a generator with an internal resistance of 50 Ω .

❖ *Solution*

$$\begin{aligned}n &= \frac{1}{2} \times \frac{\log_{10}(10^{30/10} - 1) - \log_{10}(10^{3/10} - 1)}{\log_{10}(40/10)} \\ &= \frac{1}{2} \times \frac{\log_{10}(10^3 - 1) - \log_{10}(1.9953 - 1)}{\log_{10}(4)} \approx \frac{0.5 \times 3}{0.6} \approx 2.5\end{aligned}$$

Therefore, $n = 3$ elements will be needed for this maximally flat filter.


LP Butterworth example

$$g_0 = g_4 = 1$$
$$g_1 = 2 \sin \frac{(2-1)\pi}{2 \times 3} = 2 \sin \frac{\pi}{6} = 1$$
$$g_2 = 2 \sin \frac{(4-1)\pi}{2 \times 3} = 2 \sin \frac{\pi}{2} = 2$$
$$g_3 = 2 \sin \frac{(6-1)\pi}{2 \times 3} = 2 \sin \frac{5\pi}{6} = 1$$

scaling element values

$$L_1 = L_3 = 50 \times \frac{1}{2\pi \times 10^7} \text{H} = 795.77 \text{ nH}$$
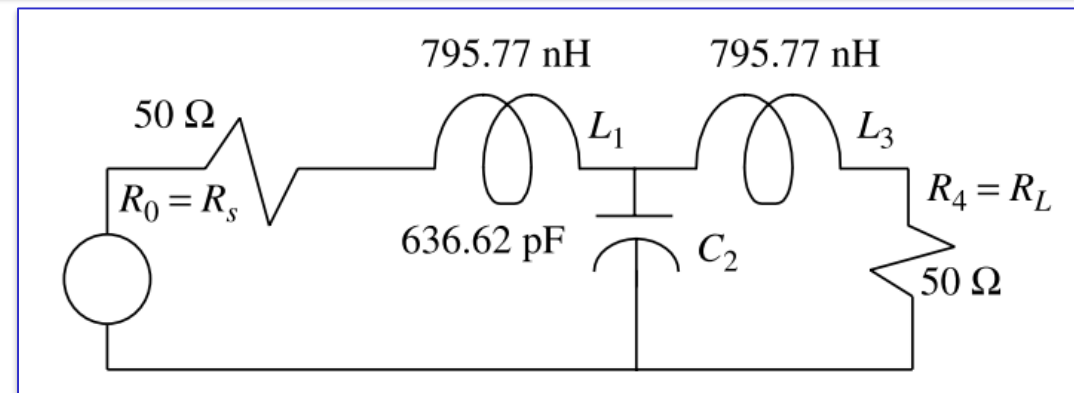
$$C_2 = \frac{1}{50} \times \frac{2}{2\pi \times 10^7} \text{F} = 636.62 \text{ pF}$$



LP Chebyshev example

❖ *Example*

- Design a low-pass Chebyshev filter that may have ripples no more than 0.01 dB in its pass-band. The filter must pass all frequencies up to 100 MHz and attenuate the signal at 400 MHz by at least 5 dB. The load and the source resistance are of 75 Ω each.

❖ *Solution*

Since $G_r = 0.01$ and $L = 5\text{dB}$

$$m = \frac{\cosh^{-1} \sqrt{(10^{0.5} - 1)/(10^{0.001} - 1)}}{\cosh^{-1}(4)} = 2$$

Since we want a symmetrical filter with 75 Ω on each side, we select $m = 3$.

LP Chebyshev example

$$g_0 = g_4 = 1$$

$$a_1 = \sin \frac{(2-1)\pi}{2 \times 3} = \sin \frac{\pi}{6} = 0.5$$

$$a_2 = \sin \frac{(4-1)\pi}{2 \times 3} = \sin \frac{\pi}{2} = 1$$

$$a_3 = \sin \frac{(6-1)\pi}{2 \times 3} = \sin \frac{5\pi}{6} = 0.5$$

$$\xi = \ln \left(\coth \frac{0.01}{17.37} \right) = 7.5$$

$$\chi = \sinh \frac{7.5}{6} = 1.6019$$

$$b_1 = 1.6019^2 + \sin^2 \frac{\pi}{3} = 3.316$$

$$b_2 = 1.6019^2 + \sin^2 \frac{2\pi}{3} = 3.316$$

$$b_3 = 1.6019^2 + \sin^2 \frac{3\pi}{3} = 2.566$$

LP Chebyshev example

$$g_0 = g_4 = 1$$

$$g_1 = \frac{2 \times 0.5}{1.6019} = 0.62425$$


$$g_2 = \frac{4 \times 0.5 \times 1}{3.316 \times 0.62425} = 0.9662$$

$$g_3 = \frac{4 \times 1 \times 0.5}{3.316 \times 0.9662} = 0.62425$$

scaling element values


$$L_1 = L_3 = \frac{75 \times 0.62425}{2\pi \times 10^8} \text{H} = 74.5155 \text{ nH}$$
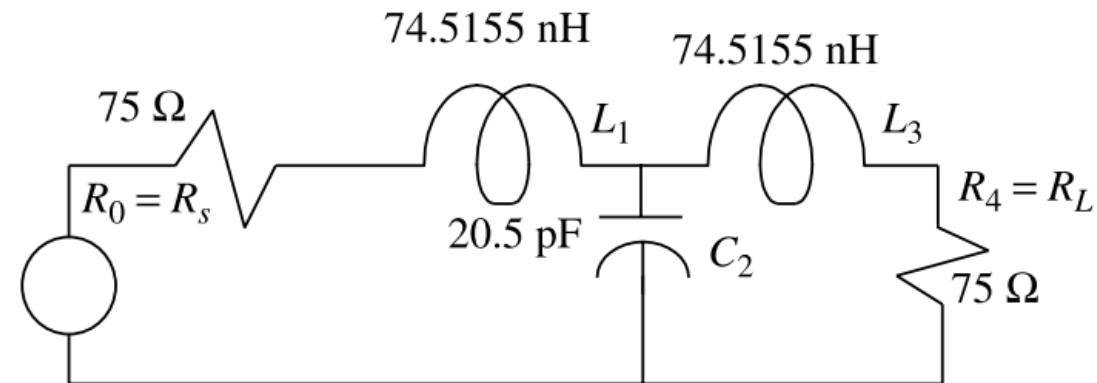
$$C_2 = \frac{1}{75} \times \frac{1}{2\pi \times 10^8} \times 0.9662 \text{F} = 20.5 \text{ pF}$$



High Pass Filter

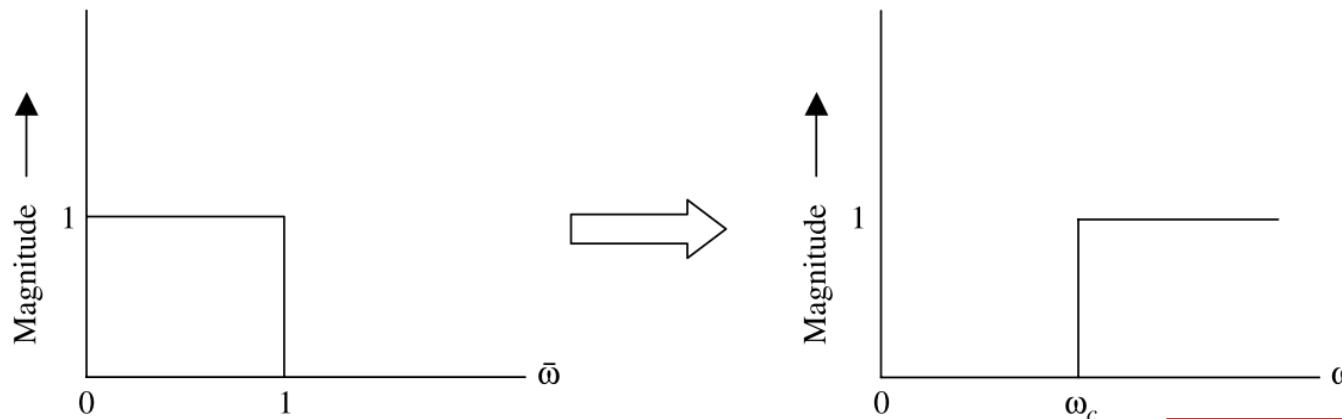- A high-pass filter can be designed by
 - ❖ transforming the low-pass prototype
 - ❖ The frequency transformation is shown below



- ❖ The frequency transformation is thus

$$\bar{\omega} = \frac{\omega_c}{\omega}$$

High Pass Filter

- Thus, inductors and capacitors will change their places.
 - ❖ Inductors will replace the shunt capacitors of the low-pass filter and
 - ❖ capacitors will be connected in series, in place of inductors.
- The elements are determined as follows:

$$C_{\text{HP}} = \frac{1}{\omega_c g_L}$$

$$L_{\text{HP}} = \frac{1}{\omega_c g_C}$$

- Capacitor C_{HP} and inductor L_{HP}
 - ❖ are then scaled as required by the load and source resistance.

High Pass Filter

❖ *Example*

- Design a high-pass Chebyshev filter with pass-band ripple magnitude less than 0.01 dB. It must pass all frequencies over 100 MHz and exhibit at least 5 dB of attenuation at 25 MHz. Assume that the load and source resistances are at 75 Ω each.

❖ *Solution*

The low-pass filter designed in Example 9.7 provides the initial data for this high-pass filter. With $m = 3$, $g_L = 0.62425$, and $g_C = 0.9662$,

$$C_{\text{HP}} = \frac{1}{2\pi \times 10^8 \times 0.62425} \text{ F} = 2.5495 \text{ nF}$$



High Pass Filter

$$L_{\text{HP}} = \frac{1}{2\pi \times 10^8 \times 0.9662} \text{ H} = 1.6472 \text{ nH}$$

❖ applying the resistance scaling, we get


$$C_1 = C_3 = \frac{2.5495}{75} \text{ nF} \approx 34 \text{ pF}$$
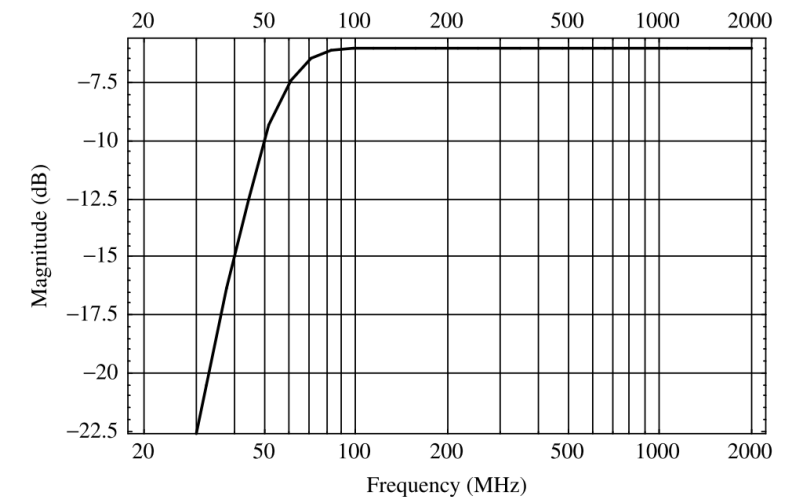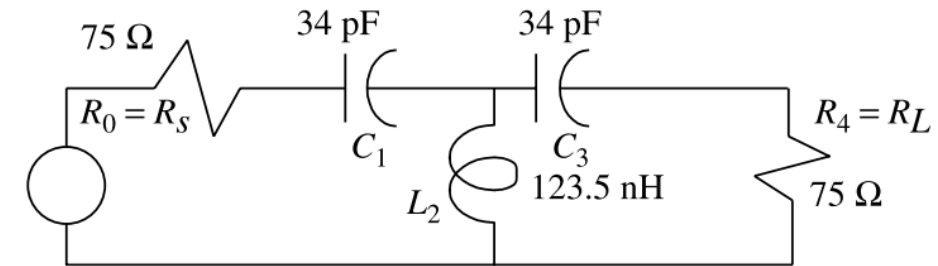
$$L_2 = 75 \times 1.6472 \text{ nH} = 123.5 \text{ nH}$$



Band Pass Filter

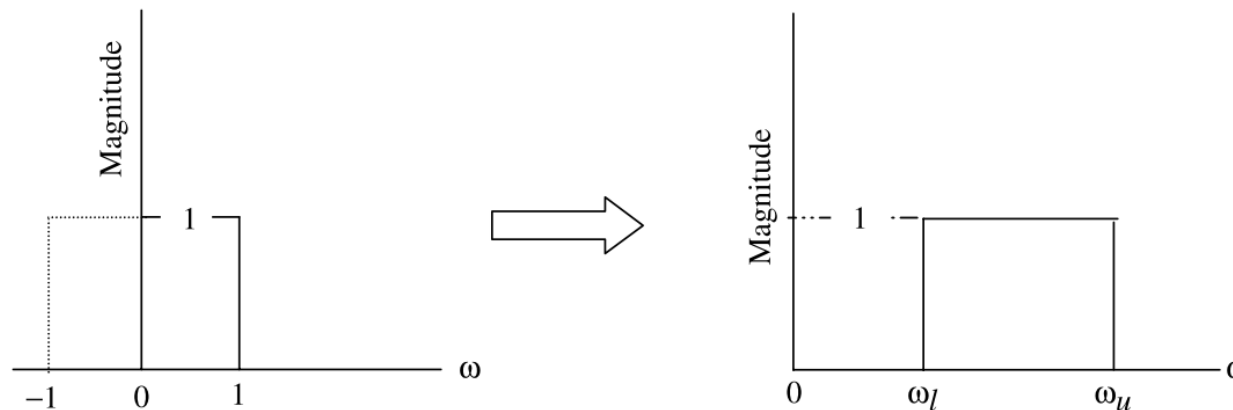- A band-pass filter can be designed by
 - ❖ transforming the low-pass prototype
 - ❖ The frequency transformation is shown below



$$\omega_0 = \sqrt{\omega_l \times \omega_u}$$

- ❖ The frequency transformation is thus

$$\omega = \frac{1}{\omega_u - \omega_l} \frac{\omega^2 - \omega_0^2}{\omega}$$

Band Pass Filter

□ This transformation

- ❖ replaces the series inductor of low-pass prototype with
 - an inductor L_{BP1} and a capacitor C_{BP1} that are connected in series.
- ❖ The components values are determined as follows:

$$C_{BP1} = \frac{\omega_u - \omega_l}{\omega_o^2 g_L}$$

$$L_{BP1} = \frac{g_L}{\omega_u - \omega_l}$$

□ Also, capacitor C_{BP2} connected in parallel with inductor L_{BP2}

- ❖ will replace the shunt capacitor of the low-pass prototype.

Band Pass Filter

- The components values are determined as follows:

$$L_{\text{BP2}} = \frac{\omega_u - \omega_l}{\omega_o^2 g_C}$$

$$C_{\text{BP2}} = \frac{g_C}{\omega_u - \omega_l}$$

- These elements need to be scaled further as desired by the load and source resistance.

Band Pass Filter

❖ *Example*

- Design a bandpass Chebyshev filter that exhibits no more than 0.01-dB ripples in its passband. It must pass signals in the frequency band 10 to 40 MHz with zero insertion loss. Assume that the load and source resistances are at 75 Ω each.

❖ *Solution*

$$f_o = \sqrt{f_l f_u} = \sqrt{10^7 \times 40 \times 10^6} = 20 \times 10^6 \text{ Hz}$$

- With $m = 3$, $g_L = 0.62425$, and $g_C = 0.9662$,

$$C_{\text{BP1}} = \frac{2\pi \times 10^6 (40 - 10)}{(2\pi \times 20 \times 10^6)^2 \times 0.62425} \text{ F} = 19.922 \text{ nF}$$


Band Pass Filter

$$L_{BP1} = \frac{0.62424}{2\pi \times 30 \times 10^6} \text{H} = 3.3116 \text{ nH}$$

$$L_{BP2} = \frac{2\pi \times 10^6 (40 - 10)}{(2\pi \times 20 \times 10^6)^2 \times 0.9662} \text{H} = 12.354 \text{ nH}$$

$$C_{BP2} = \frac{0.9662}{2\pi \times 30 \times 10^6} \text{F} = 5.1258 \text{ nF}$$

❖ applying the resistance scaling,

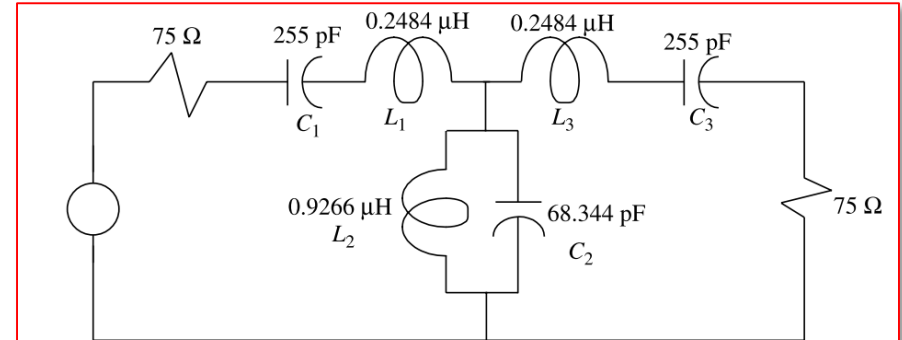


$$C_1 = C_3 = \frac{19.122}{75} \text{ nF} = 254.96 \text{ pF} \approx 255 \text{ pF}$$

$$L_1 = L_3 = 75 \times 3.3116 \text{ nH} = 0.2484 \text{ uH}$$

$$L_2 = 75 \times 12.354 \text{ nH} = 0.9266 \text{ uH}$$

$$C_2 = \frac{5.1258}{75} \text{ nF} = 68.344 \text{ pF}$$

Band Pass Filter

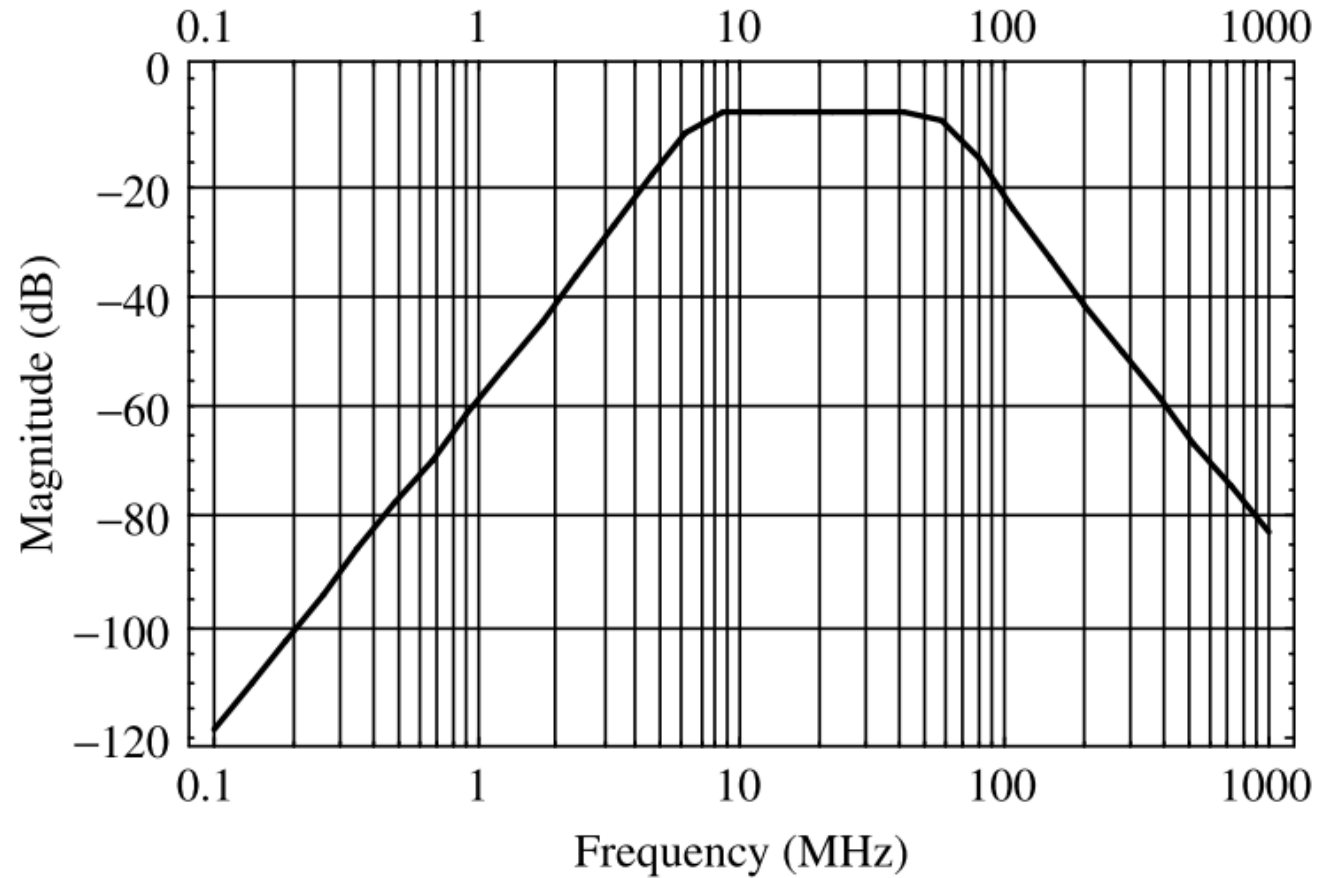


Band Stop Filter

□ A band-pass filter can be realized by

❖ transforming the low-pass prototype

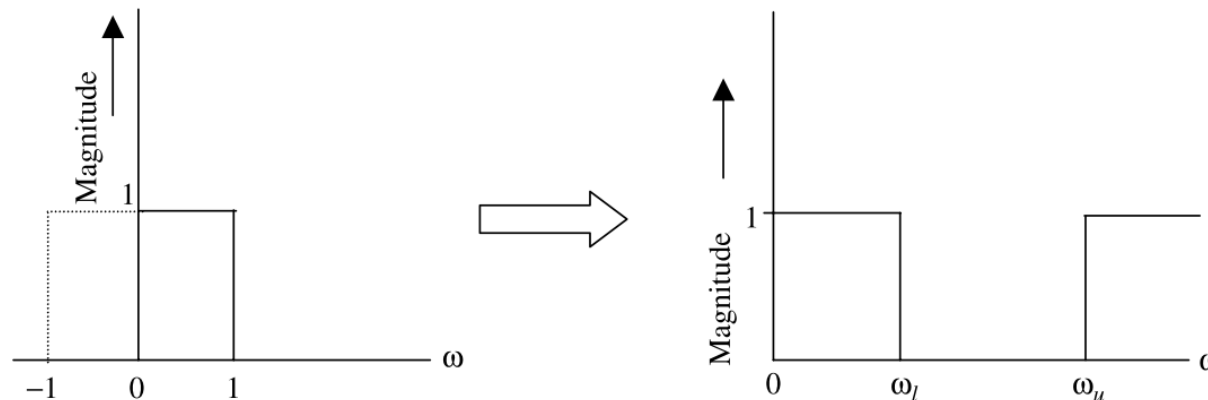❖ The frequency transformation is shown below



$$\omega_0 = \sqrt{\omega_l \times \omega_u}$$

❖ The frequency transformation is thus

$$\bar{\omega} = (\omega_u - \omega_l) \frac{\omega}{\omega^2 - \omega_0^2}$$

Band Stop Filter

□ This transformation

❖ replaces the series inductor of low-pass prototype with

➤ an inductor L_{BS1} and a capacitor C_{BS1} that are connected in parallel.

❖ The components values are determined as follows:

$$L_{BS1} = \frac{(\omega_u - \omega_l) g_L}{\omega_0^2}$$

$$C_{BS1} = \frac{1}{(\omega_u - \omega_l) g_L}$$

□ Also, C_{BS2} which is connected in series with an inductor L_{BS2} ,

❖ will replace the shunt capacitor of the low-pass prototype.

Band Stop Filter

- The components values are determined as follows:

$$L_{\text{BS2}} = \frac{1}{(\omega_u - \omega_l) g_C}$$

$$C_{\text{BS2}} = \frac{(\omega_u - \omega_l) g_C}{\omega_o^2}$$

- These elements need to be scaled further as desired by the load and source resistance.

Band Stop Filter

❖ *Example*

- Design a maximally flat bandstop filter with $n = 3$. It must stop signals in the frequency range 10 to 40 MHz and pass the rest of the frequencies. Assume that the load and source resistances are at 75Ω each.

❖ *Solution*

$$f_o = \sqrt{f_l f_u} = \sqrt{10^7 \times 40 \times 10^6} = 20 \times 10^6 \text{ Hz}$$

- With $n = 3$, $g_L = 1$, and $g_C = 2$, from previous example,

$$L_{BS1} = \frac{2\pi \times 10^6 (40 - 10)}{(2\pi \times 20 \times 10^6)^2} \times 1 \text{ H} = 11.94 \text{ nH}$$


Band Stop Filter

$$C_{BS1} = \frac{1}{2\pi \times 10^6 (40 - 10) \times 1} \text{ F} = 5.305 \text{ nF}$$

$$L_{BS2} = \frac{1}{2\pi \times 10^6 (40 - 10) \times 2} \text{ H} = 2.653 \text{ nH}$$

$$C_{BS2} = \frac{2\pi \times 10^6 (40 - 10)}{(2\pi \times 20 \times 10^6)^2} \times 2 \text{ F} = 23.87 \text{ nF}$$

❖ applying the resistance scaling,

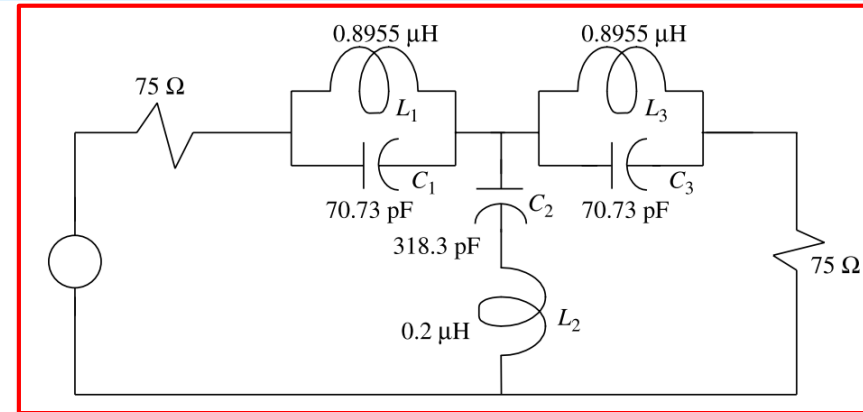

$$C_1 = C_3 = \frac{5.305}{75} \text{ nF} = 70.73 \text{ pF}$$

$$L_1 = L_3 = 75 \times 11.94 \text{ nH} = 0.8955 \text{ uH}$$

$$L_2 = 75 \times 2.653 \text{ nH} = 0.1989 \text{ uH} \approx 0.2 \text{ uH}$$

$$C_2 = \frac{23.87}{75} \text{ nF} = 318.3 \text{ pF}$$

Band Stop Filter

