

TE 474

LECTURE 2:

Transmission Line Theory

2017.01.11

Abdul-Rahman Ahmed

Transmission Line Theory



KNUST
Telecomm.
Engineering

Presentation Layout

- ❑ Transmission Line (TL) Equation
- ❑ Parameters of TL
- ❑ Reflection and Return Loss
- ❑ Smith Chart
- ❑ Coaxial Lines

Transmission Line Theory



KNUST
Telecomm.
Engineering


Transmission Line Equation

Introduction



KNUST
Telecomm.
Engineering

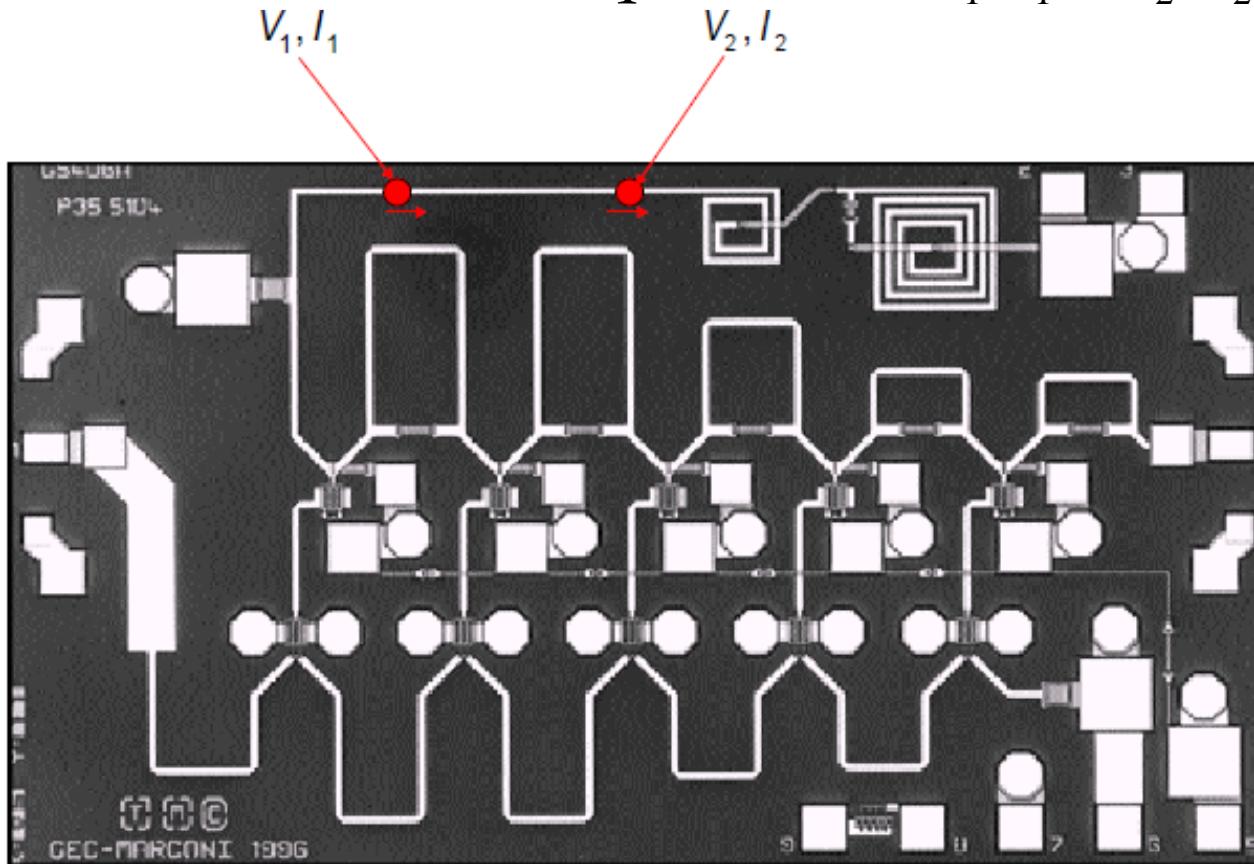
- At microwave frequencies, $V_1, I_1 \neq V_2, I_2$ respectively




Assumption

Cross section is Uniform across propagating direction

Transmission Line Parameters

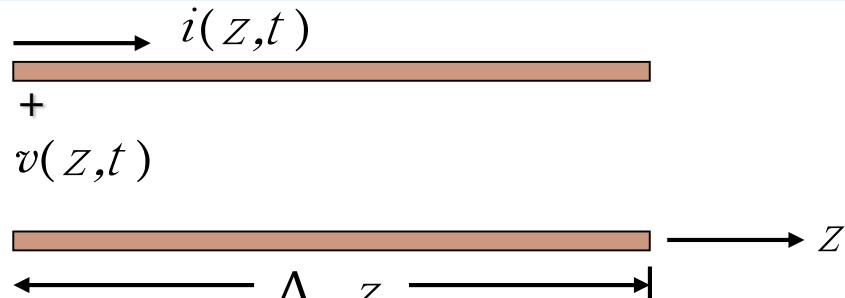

(a) Voltage and current definitions

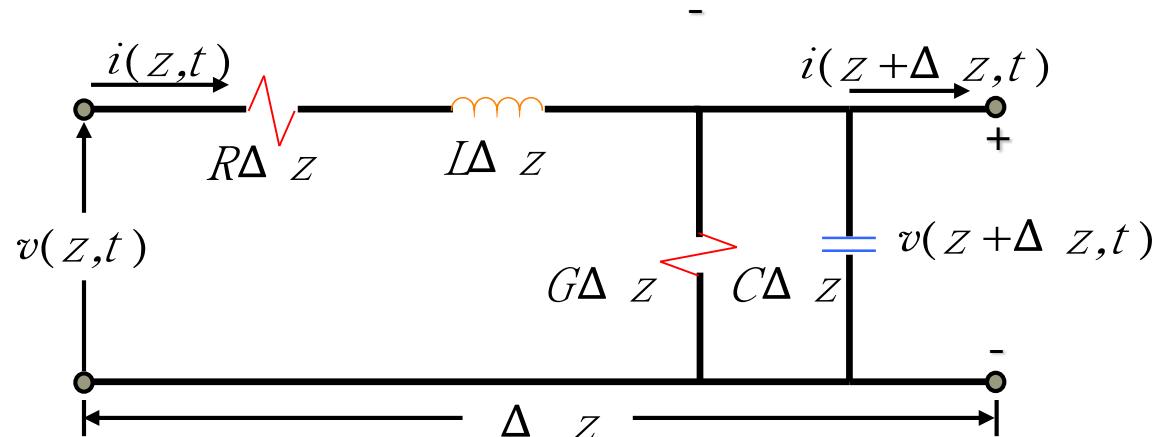

(b) Lumped-element equivalent circuit

Fig. 2.1 Incremental length of transmission line

Transmission Line Parameters




R : series resistance per unit length, for both conductors (conductor finite σ) (Ω/m)

L : series inductance per unit length, for both conductors (conductor wire's self inductance) (H/m)

G : shunt conductance per unit length (dielectric loss) (S/m)

C : shunt capacitance per unit length (capacitance between the conductors) (F/m)

Transmission Line Parameters

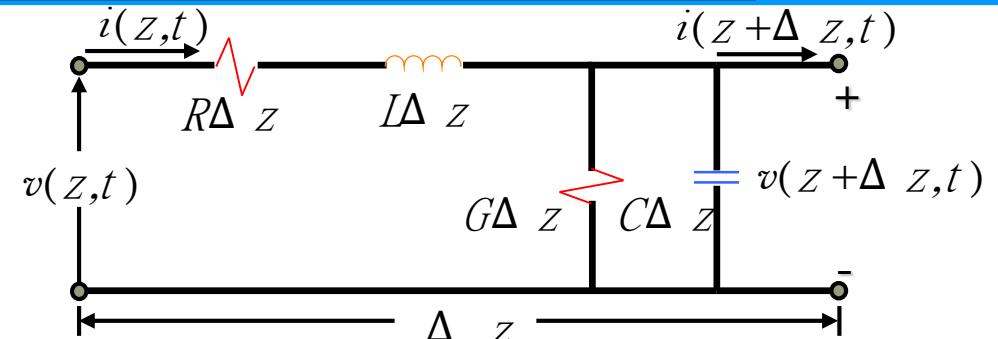

$$\text{KVL : } v(z,t) - R\Delta z i(z,t) - L\Delta z \frac{\partial i(z,t)}{\partial t} = v(z + \Delta z, t) \quad (2.1 \text{ a})$$

$$(2.1 \text{ a}) \implies \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\Delta z \rightarrow 0 \quad \frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

Telegrapher
equations

Transmission Line Parameters



Wave Propagation on a Transmission Line

$$\left. \begin{array}{l} \frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \\ \frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \end{array} \right\} \text{wave equations} \quad \begin{array}{l} (2.4 \text{ a}) \\ (2.4 \text{ b}) \end{array}$$

where $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$

Solution of (2.4) is

$$\left. \begin{array}{l} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \end{array} \right\} \quad \begin{array}{l} (2.6 \text{ a}) \\ (2.6 \text{ b}) \end{array}$$

Transmission Line Parameters



(2.6 a) into (2.3 a)

$$\left(\textcircled{2.6 a} \quad \frac{dV(z)}{dz} = -(R + j\omega L) I(z) \quad (2.3 a) \right)$$

$$-\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z} = -(R + j\omega L) I(z)$$

$$\begin{aligned} \therefore I(z) &= \frac{\gamma}{R + j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}) \\ &= \frac{1}{Z_0} (V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}) \end{aligned} \quad (2.8)$$

Z_0 : characteristic impedance

$$= \frac{R + j\omega L}{\gamma} = \frac{R + j\omega L}{\sqrt{(R + j\omega L)G + j\omega C}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Transmission Line Parameters



Lossless Line

$$\gamma = \alpha + j\beta = j\beta = j\omega\sqrt{LC} \quad (R = G = 0)$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}} \left(= \frac{V_p}{f} \right)$$

$$V_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad (2.14 \text{ a})$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad (2.14 \text{ b})$$


Transmission Line Parameters



KNUST
Telecomm.
Engineering

Terminated Lossless Transmission Line

Transmission Line Parameters

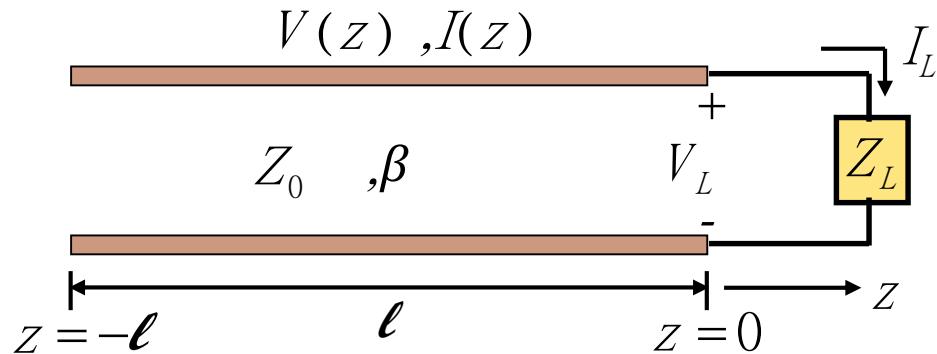

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} [V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z}]$$

At $z = 0$,

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_L}{I_L} = Z_0 \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-}$$

Transmission Line Parameters



$$\therefore V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+ = \Gamma V_0^+$$

where $\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$: voltage reflection coefficient

[Similar to $\Gamma = \frac{\eta_L - \eta_0}{\eta_L + \eta_0}$]
for plane wave

$\Gamma = 0$ (No reflection)



$$\therefore V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$$

Transmission Line Parameters



Time-average power flow along the line

$$\begin{aligned} P_{av} &= \frac{1}{2} R e[V(z)I^*(z)] \\ &= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \left\{ 1 - \underbrace{\Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z}}_{\text{purely imaginary}} - |\Gamma|^2 \right\} \\ &= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2) \end{aligned}$$

Return Loss (RL)

$$RL = -20 \log |\Gamma| (\text{dB})$$

$\Gamma = 0$; match

$RL = \infty \text{ dB}$

$|\Gamma| = 1$; open or short

$RL = 0 \text{ dB}$

Transmission Line Parameters



V_{\max} , V_{\min} , SWR

$$\begin{aligned}V(z) &= V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}) = V_0^+ (e^{-j\beta z} + |\Gamma| e^{j(\beta z + \theta)}) \\&\quad (\because \Gamma = |\Gamma| e^{j\theta}) \\&= V_0^+ [(\cos \beta z - j \sin \beta z) + |\Gamma| \{ \cos(\beta z + \theta) + j \sin(\beta z + \theta) \}] \\&= V_0^+ [(\cos \beta z + |\Gamma| \cos(\beta z + \theta) + j \{ |\Gamma| \sin(\beta z + \theta) - \sin \beta z \})]\end{aligned}$$

$$\begin{aligned}\therefore |V(z)| &= |V_0^+| \sqrt{\{ \cos \beta z + |\Gamma| \cos(\beta z + \theta) \}^2 + \{ |\Gamma| \sin(\beta z + \theta) - \sin \beta z \}^2} \\&= |V_0^+| \sqrt{1 + 2|\Gamma| \cos \beta z \cdot \cos(\beta z + \theta) - 2|\Gamma| \sin \beta z \cdot \sin(\beta z + \theta) + |\Gamma|^2} \\&= |V_0^+| \sqrt{1 + 2|\Gamma| \cos(2\beta z + \theta) + |\Gamma|^2}\end{aligned}$$

Transmission Line Parameters



$$\therefore V_{\text{max}} = |V_0^+| (1 + |\Gamma|)$$
$$(\cos(2\beta z + \theta) = 1)$$

→ distance between successive maxima is $\lambda / 2$

$$V_{\text{min}} = |V_0^+| (1 - |\Gamma|)$$
$$(\cos(2\beta z + \theta) = -1)$$

→ distance between successive minima is $\lambda / 2$

(Voltage) Standing Wave Ratio : SWR or VSWR

$$\text{SWR} = \frac{V_{\text{max}}}{V_{\text{min}}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$1 \leq \text{SWR} < \infty, \text{SWR} = 1 \quad |\Gamma| = 0 \text{ and matched}$$

Transmission Line Parameters



Reflection Coefficient at

$$z = -\ell$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad \text{at} \quad z = -\ell$$

$$\Gamma(-\ell) = \frac{V^-(-\ell)}{V^+(-\ell)} = \frac{V_0^- e^{-j\beta \ell}}{V_0^+ e^{j\beta \ell}} = \frac{V_0^-}{V_0^+} e^{-j2\beta \ell} = \Gamma(0) e^{-2j\beta \ell}$$

Input impedance at

$$z = -\ell$$

$$Z_{in} = \frac{V(-\ell)}{I(-\ell)} = \frac{V_0^+ (e^{j\beta \ell} + \Gamma e^{-j\beta \ell})}{V_0^+ (e^{j\beta \ell} - \Gamma e^{-j\beta \ell})} Z_0 = \frac{1 + \Gamma e^{-j2\beta \ell}}{1 - \Gamma e^{-j2\beta \ell}} Z_0$$

$$= Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$


(refer to (2.44))

$$\left[\because \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \right]$$

Special Cases of Lossless Terminated Lines



① Short-circuited Termination

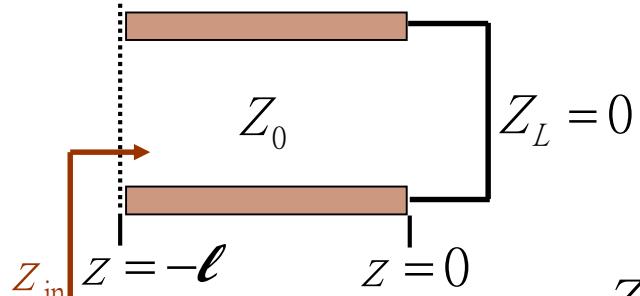

$$Z_L = 0 \quad \therefore \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

$$V(z) = V_0^+ (e^{-j\beta z} - e^{j\beta z}) = -2jV_0^+ \sin\beta z$$


$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} + e^{j\beta z}) = \frac{2V_0^+}{Z_0} \cos\beta z$$

$$Z_{in} = \frac{V(-\ell)}{I(-\ell)} = jZ_0 \tan\beta \ell$$

Special Cases of Lossless Terminated Lines



② Open-circuited Termination

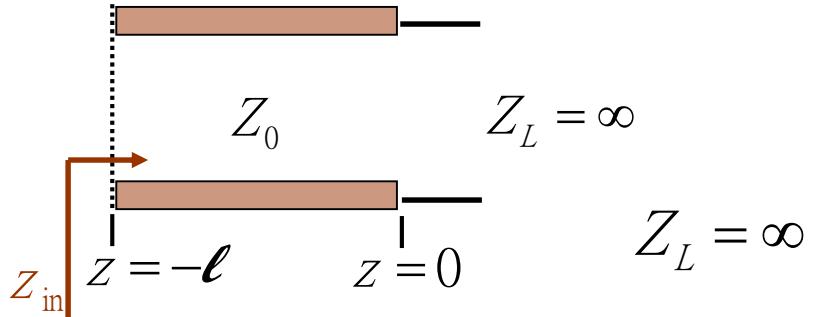

$$Z_L = \infty$$

$$\therefore \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$

$$V(Z) = V_0^+ (e^{-j\beta Z} + e^{j\beta Z}) = 2V_0^+ \cos \beta Z$$

$$I(Z) = \frac{V_0^+}{Z_0} (e^{-j\beta Z} - e^{j\beta Z}) = \frac{-2jV_0^+}{Z_0} \sin \beta Z$$

$$Z_{in} = -jZ_0 \cot \beta \ell$$



Special Cases of Lossless Terminated Lines



$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$

$$\ell = \frac{\lambda}{2} \quad \beta \ell = \frac{2\pi}{\lambda} \times \frac{\lambda}{2} = \pi \quad \therefore Z_{in} = Z_L$$
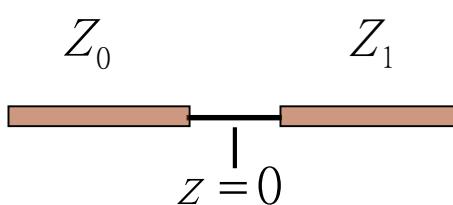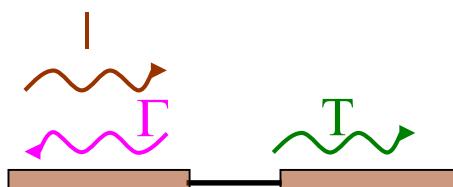
$$\ell = \frac{\lambda}{4} \quad \beta \ell = \frac{\pi}{2} \quad \therefore Z_{in} = \frac{Z_0^2}{Z_L} \quad \text{quarter-wave transformer}$$



$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$z < 0 \quad V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$z > 0 \quad V(z) = V_0^+ T e^{-j\beta z}$$

$z = 0$ Since $V(0)$ must be same,

$$T = 1 + \Gamma = 1 + \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{2Z_1}{Z_1 + Z_0}$$

Smith Chart



KNUST
Telecomm.
Engineering

- graphical aid useful for solving t-line problems.
- Developed by P. Smith in 1939 at Bell Telephone Laboratories
- Enables visualization of transmission line problems without requiring much calculation
- Smith chart to the M/W engineer is useful for developing intuition of transmission line problems.

Smith Chart



KNUST
Telecomm.
Engineering

Example: Basic Smith Chart Operations


Load impedance : $130 + j90 \Omega$

X'tics impedance of t-line: 50Ω

Length of line: 0.3λ

$\Gamma(0)$, $\Gamma(-0.\lambda)$, Z_{in} , SWR on the line, Return loss?

Smith Chart-Transmission Line Problem

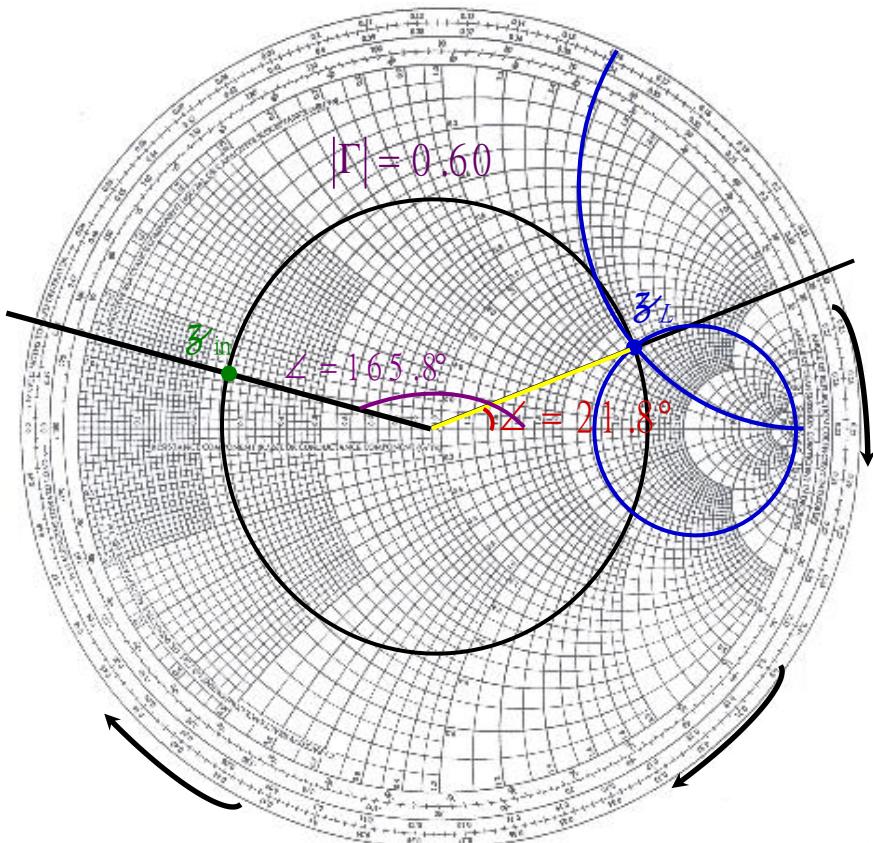


- ① $\mathcal{Z}_L = \frac{Z_L}{Z_0} = 2.60 + j1.80$ plotted.
- ② Using Compass or rule
 $|\Gamma| = 0.6$, SWR = 3.98,
 $RL = 4.4\text{dB}$, $\theta = 21.8^\circ$
- ③ 0.220λ Direction wavelengths-
toward-generator move
0.3λ to 0.520λ
With period of 0.5λ
Equivalent to 0.020λ
- ④ Reading
 $\mathcal{Z}_{in} = 0.255 + j0.117$
 $\therefore Z_{in} = \mathcal{Z}_{in}Z_0 = 12.7 + j5.8$
- ⑤ $|\Gamma(-0.3\lambda)| = |\Gamma(0)|$ $\theta(-0.3\lambda) = 165.8^\circ$

Measurement of Z_o

Impedance method(High Frequency)

$$\text{End Terminal Open } Z_{OPEN} = \frac{1}{j\omega C_m l}$$
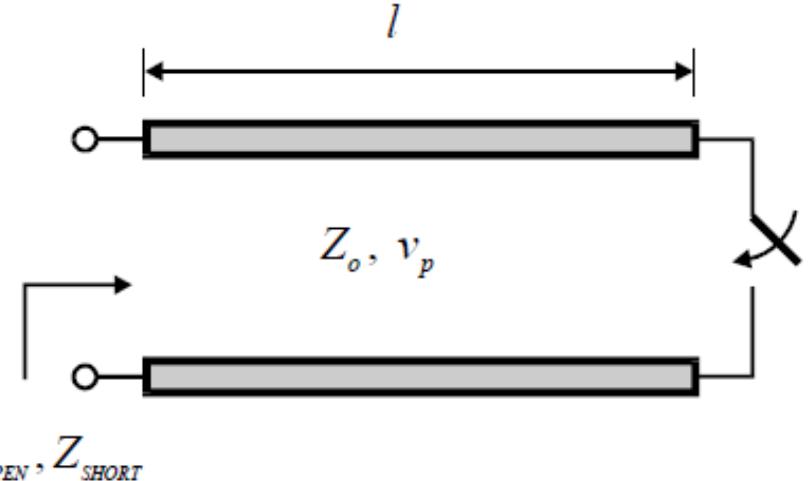
$$\text{End Terminal Short } Z_{SHORT} = j\omega L_m l$$



$$Z_o = \sqrt{\frac{L}{C}} = \sqrt{Z_{OPEN} \cdot Z_{SHORT}}$$

$$v_p = \frac{1}{\sqrt{LC}} = \frac{1}{\omega l} \sqrt{\frac{Z_{OPEN}}{Z_{SHORT}}}$$

Coaxial Transmission Lines

Coaxial Lines




KNUST
Telecomm.
Engineering

- Used for measurement
 - ❖ Construction: Connector, Cable and Adapter

- Cable:
 - ❖ Flexible, Semi-Rigid, Handy reformable

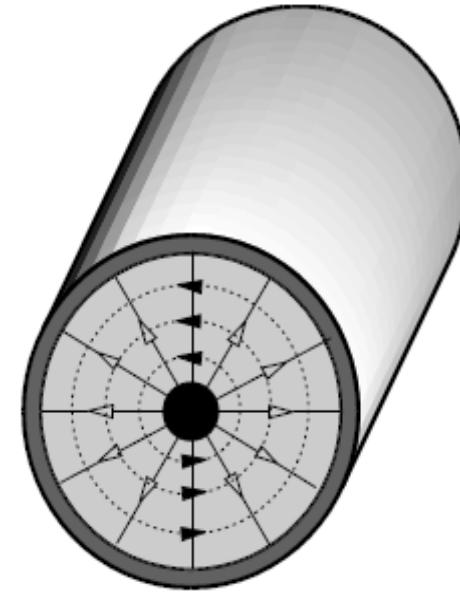
- Connectors:
 - ❖ BNC, TNC, SMA
 - ❖ Precision; 7.0mm, , 3.5mm, 2.9mm, 2.4mm, 1.0mm



Coaxial Lines



KNUST
Telecomm.
Engineering

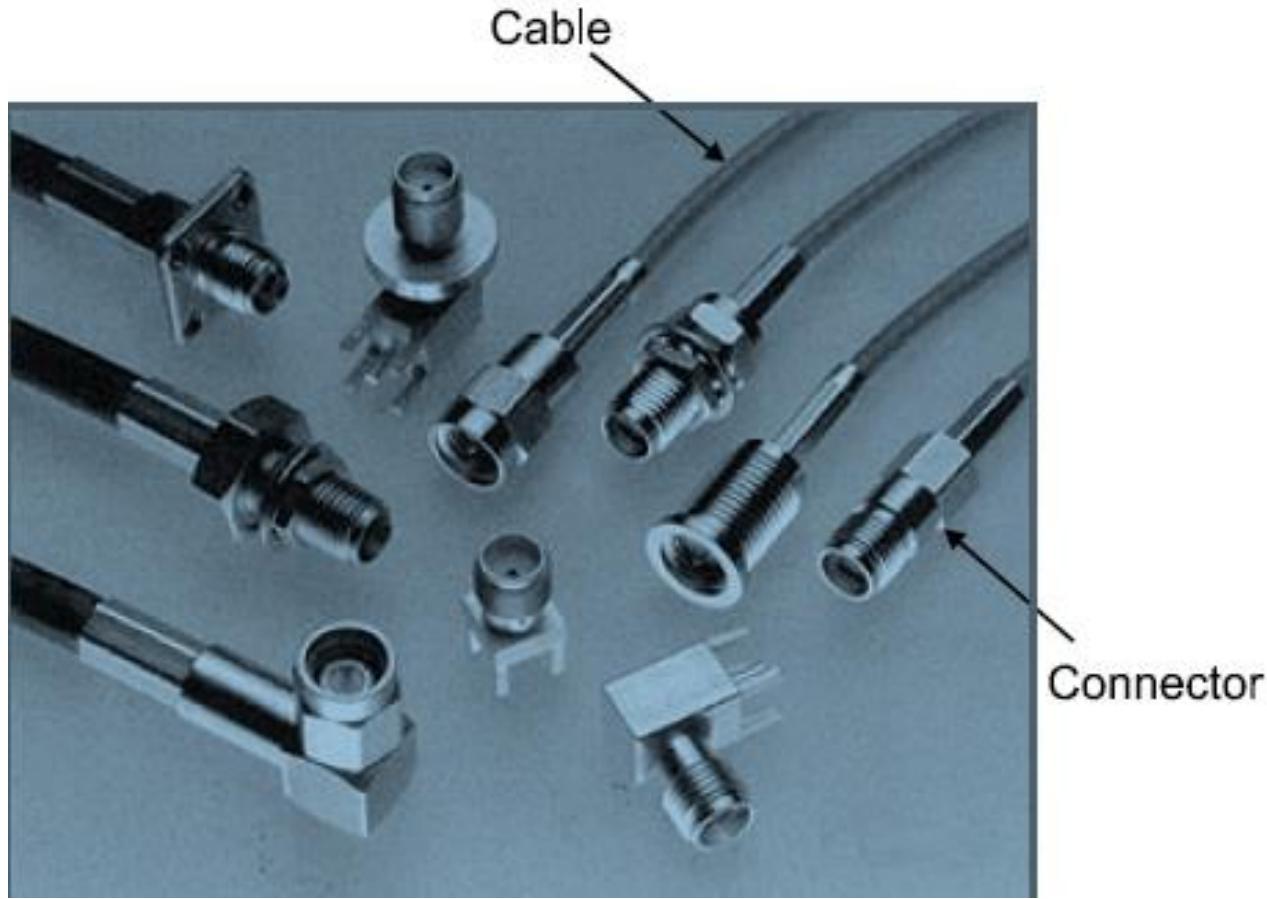

Photograph of Coaxial Transmission

Coaxial Line Connectors



KNUST
Telecomm.
Engineering

□SMA Adaptors




□BNC, TNC, SMA



Photograph of Coaxial Connectors

Simulation Project 1

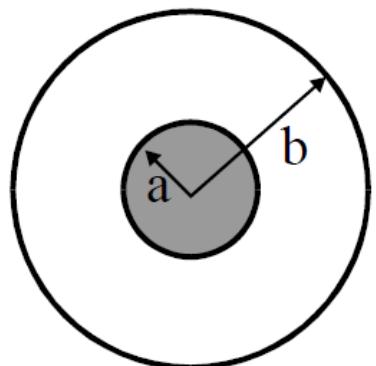- ❖ A kind of coaxial cable RG-142 has an inner radius a of 0.035 inch and an outer radius b , of 0.116 inch. By using ADS, follow the open -short procedure and express the characteristics impedance of the coaxial cable in terms of the ratio a/b , where a and b are the inner and outer radii respectively shown in Fig. 3E.3 below. Compare the results obtained with that obtained from the formula



$$Z_o = 60 \sqrt{\frac{\mu_r}{\epsilon_r}} \ln\left(\frac{b}{a}\right)$$