
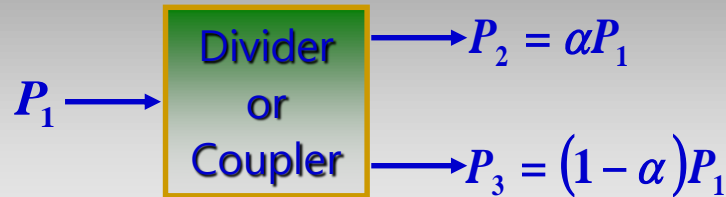


Ch. 7 Power Dividers and Directional Couplers

Power divider or combiner

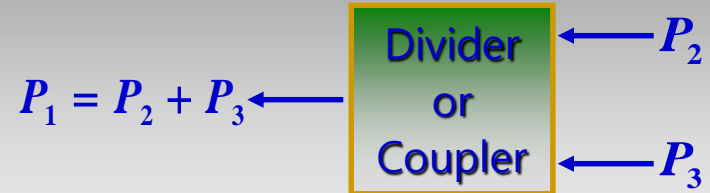


<Power division>




<Power combining>


- T-junctions (3-port network)

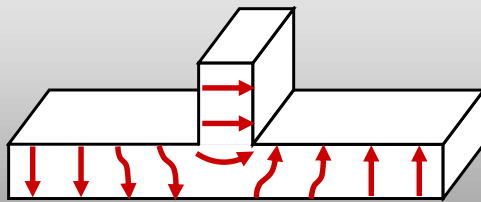

< E-plane waveguide T >

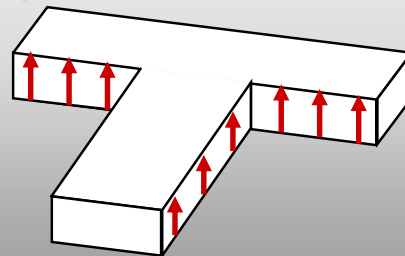


<H-plane waveguide T >

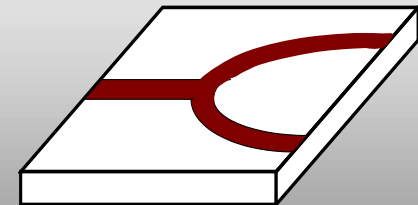


<Microstrip T-junction>

VII- 1

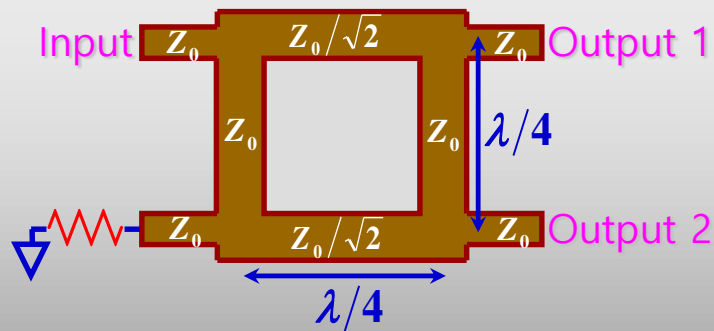- Directional couplers (4-port network)
 - arbitrary power division
(10 dB, 20 dB, 3 dB, etc.)
- Hybrid junctions (4-port network)
 - equal power division (3 dB)


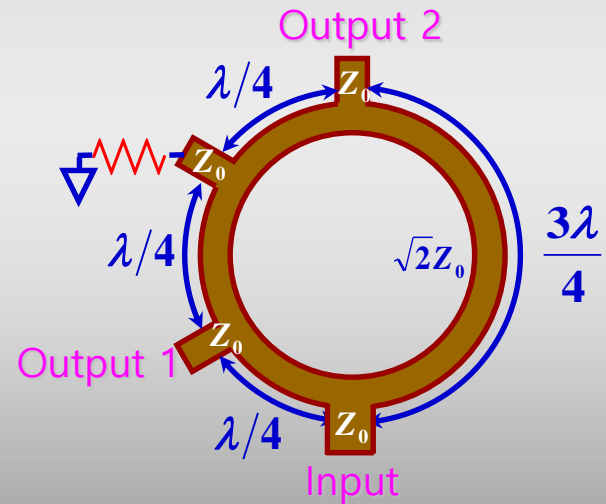
< **90°** phase difference >
(quadrature hybrid)



< **180°** phase difference >
(ring hybrid)

HISTORY

1940

- US MIT Radiation Laboratory developed mainly waveguide-type coupler, power divider, T junction etc.

Mid 1950~ 1960

- development of devices for mainly planar stripline and also microstrip circuits. (Wilkinson divider, branch line hybrid, coupled line directional coupler etc)

7.1 Basic Properties of Dividers and Couplers

Three-Port Networks (T-junctions)

$[S]$ of an arbitrary 3-port network

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} \quad (9 \text{ independent elements})$$

If the component is passive and contains no anisotropic materials,

① network is reciprocal and $S_{ij} = S_{ji}$ ($[S]$ is symmetric)
(Recall)

If the component is lossless and all ports are matched,

② $[S^*]'[S] = [U]$ ($[S]$ is a unitary matrix)
(Recall)

③ $S_{ii} = 0$

From conditions ①, ③

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} \Rightarrow [S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

From conditions ②

$$[S^*]^t [S] = [U] \Rightarrow \begin{bmatrix} 0 & S_{12}^* & S_{13}^* \\ S_{12}^* & 0 & S_{23}^* \\ S_{13}^* & S_{23}^* & 0 \end{bmatrix} \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$|S_{12}|^2 + |S_{13}|^2 = 1, \quad |S_{12}|^2 + |S_{23}|^2 = 1, \quad |S_{13}|^2 + |S_{23}|^2 = 1 \quad (7.3 \text{ a~c})$$

$$S_{13}^* S_{23} = 0 \text{ (r 1 c 2)}, \quad S_{23}^* S_{12} = 0 \text{ (r 3 c 1)}, \quad S_{12}^* S_{13} = 0 \text{ (r 2 c 3)} \quad (7.3 \text{ d~f})$$

from (7.3 d~f) S_{13}, S_{23}, S_{12} 2 out of the 3 parameters must be 0.

In that case however (7.3 a~c) will not be satisfied.

∴ A Lossless, reciprocal 3-port network cannot be matched at all ports:
 - 3 port, Lossless, reciprocal, all ports matched: Not physically realizable

However, relaxing one of the 3 conditions makes it physically realizable VII- 7

Circulator

A key physically realizable 3-port network.
(matched, lossless, but nonreciprocal)



$$[S] = \begin{bmatrix} \mathbf{0} & S_{12} & S_{13} \\ S_{21} & \mathbf{0} & S_{23} \\ S_{31} & S_{32} & \mathbf{0} \end{bmatrix}$$

$$[S^*]^t [S] = \begin{bmatrix} \mathbf{0} & S_{21}^* & S_{31}^* \\ S_{12}^* & \mathbf{0} & S_{32}^* \\ S_{13}^* & S_{23}^* & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{0} & S_{12} & S_{13} \\ S_{21} & \mathbf{0} & S_{23} \\ S_{31} & S_{32} & \mathbf{0} \end{bmatrix} = \begin{bmatrix} \mathbf{1} & \mathbf{0} & \mathbf{0} \\ \mathbf{0} & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{0} & \mathbf{1} \end{bmatrix} = [U] \text{ from this,}$$

$$S_{31}^* S_{32} = \mathbf{0} \text{ (r 1 c 2)} \quad , \quad S_{21}^* S_{23} = \mathbf{0} \text{ (r 1 c 3)} \quad , \quad S_{12}^* S_{13} = \mathbf{0} \text{ (r 2 c 3)}$$

(7.5 a~c)

$$|S_{21}|^2 + |S_{31}|^2 = \mathbf{1} \quad , \quad |S_{12}|^2 + |S_{32}|^2 = \mathbf{1} \quad , \quad |S_{13}|^2 + |S_{23}|^2 = \mathbf{1}$$


(7.5 d~f)

VII- 8


For equations (7.5 a~f) to be satisfied,

$$S_{12} = S_{23} = S_{31} = 0 \quad , \quad |S_{21}| = |S_{32}| = |S_{13}| = 1 \quad (7.6 \text{ a})$$

$$\text{or} \quad S_{21} = S_{32} = S_{13} = 0 \quad , \quad |S_{12}| = |S_{23}| = |S_{31}| = 1 \quad (7.6 \text{ b})$$

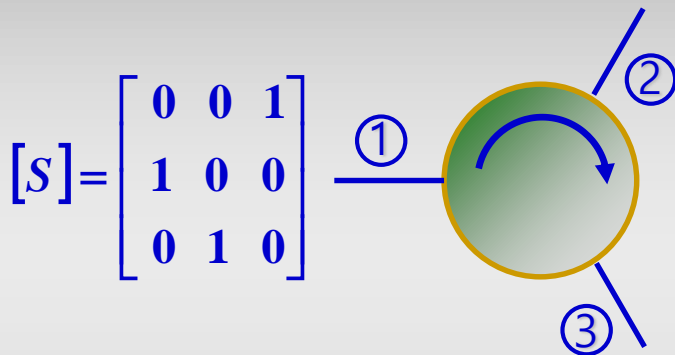

<Clockwise circulation>

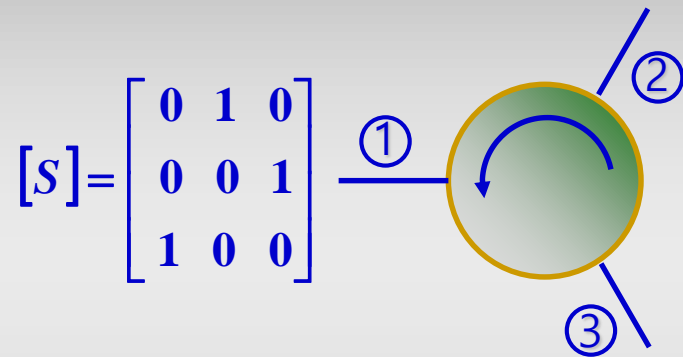

<Counterclockwise circulation>

For this example of Physically realizable 3-port network

- If Lossless, reciprocal only 2 ports matched
- If Matched, reciprocal , then lossy circuit: resistive divider

Four-Port Networks (Directional Couplers)

If the 4-port network is matched, reciprocal, and lossless

$$[S^*]^t [S] = [U] \quad \text{must be satisfied}$$

$$\begin{bmatrix} 0 & S_{12}^* & S_{13}^* & S_{14}^* \\ S_{12}^* & 0 & S_{23}^* & S_{24}^* \\ S_{13}^* & S_{23}^* & 0 & S_{34}^* \\ S_{14}^* & S_{24}^* & S_{34}^* & 0 \end{bmatrix} \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

$$S_{13}^* S_{23} + S_{14}^* S_{24} = 0 \quad (\text{r } 1 \text{ c } 2) \quad , \quad S_{14}^* S_{13} + S_{24}^* S_{23} = 0 \quad (\text{r } 4 \text{ c } 3) \quad (7.10 \text{ a~b})$$

Multiply (7.10 a) by S_{24}^* and (7.10 b) by S_{13}^* and subtract the results

$$S_{14}^* (|S_{13}|^2 - |S_{24}|^2) = 0 \quad (7.11)$$

Similarly

$$S_{12}^* S_{23} + S_{14}^* S_{34} = 0 \quad (\text{r } 1 \text{ c } 3) \quad , \quad S_{14}^* S_{12} + S_{34}^* S_{23} = 0 \quad (\text{r } 4 \text{ c } 2) \quad (7.12 \text{ a~b})$$

VII- 10


Multiply (7.12 a) by S_{12} and (7.12 b) by S_{34} and subtract the results

$$S_{23} \left(|S_{12}|^2 - |S_{34}|^2 \right) = 0 \quad (7.13)$$

The only way to satisfy (7.11) and (7.13) is

$$S_{14} = S_{23} = 0$$

(x,tics of directional coupler)

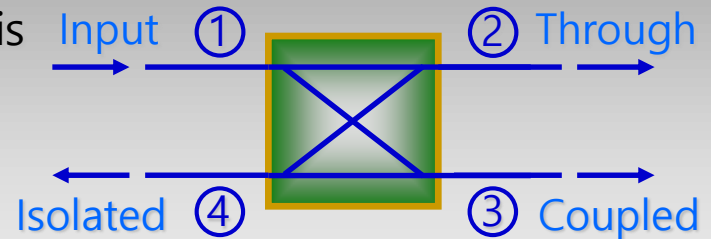

With this conditions, equations for the principal diagonal are:

$$|S_{12}|^2 + |S_{13}|^2 = 1, \quad |S_{12}|^2 + |S_{24}|^2 = 1, \quad |S_{13}|^2 + |S_{34}|^2 = 1, \quad |S_{24}|^2 + |S_{34}|^2 = 1 \quad (7.14 \text{ a~d})$$

Thus, from (7.14 a, b), $|S_{13}| = |S_{24}|$ and

$$\text{from (7.14 b, d)} \quad |S_{12}| = |S_{34}|$$

For simplicity, set. $S_{12} = S_{34} = \alpha$, $S_{13} = \beta e^{j\theta}$, $S_{24} = \beta e^{j\phi}$


Multiplying row 2 by column 3 $S_{12}^* S_{13} + S_{24}^* S_{34} = 0$ and substituting above,

$$\alpha \beta e^{j\theta} + \alpha \beta e^{-j\phi} = 0 \quad \Rightarrow \quad \therefore e^{j\theta} + e^{-j\phi} = 0$$

Two practically useful coupler $\theta = \phi = \pi/2$ and $\theta = 0, \phi = \pi$


① Symmetrical coupler
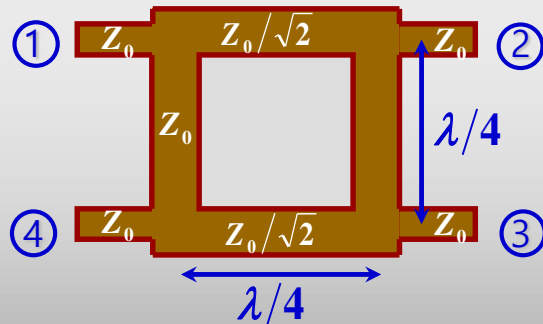
$$(\theta = \phi = \pi/2) \quad [S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$



② Assymmetrical coupler
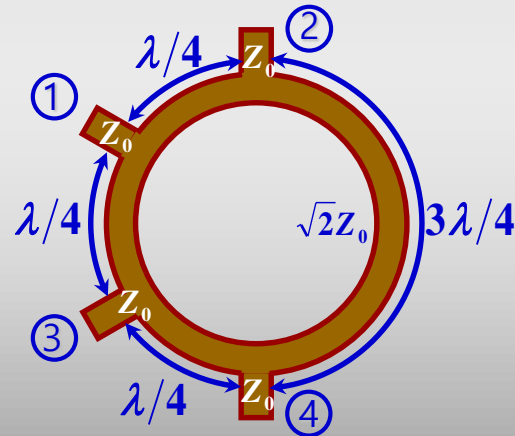
$$(\theta = 0, \phi = \pi) \quad [S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$




In both cases. $\alpha^2 + \beta^2 = 1$

In conclusion, a matched, reciprocal, lossless 4-port network is a directional coupler.

II- 12

Directional coupler

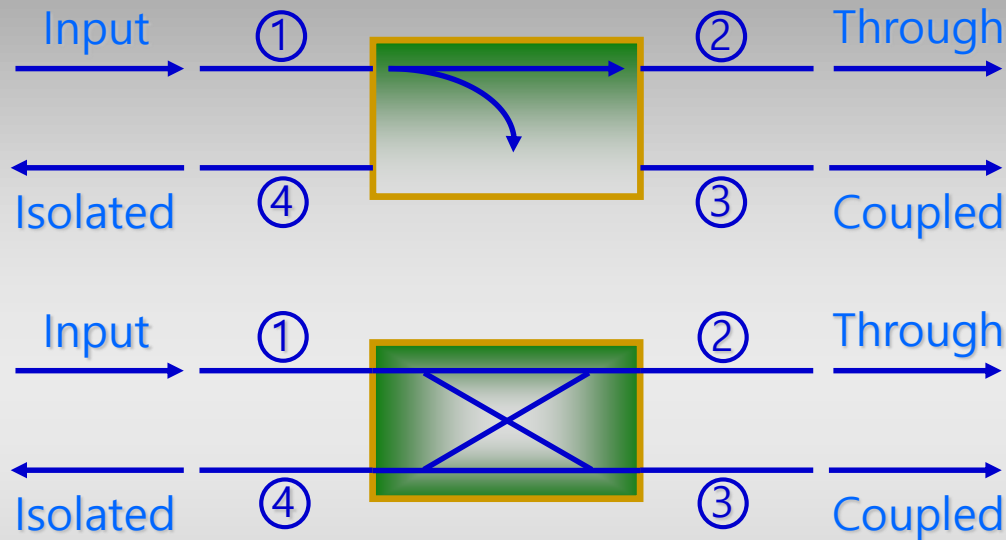


Port 1 : Power input port

Port 3 : coupled port with coupling factor $|S_{13}|^2 = \beta^2$

Port 2 : remaining power is $|S_{12}|^2 = \alpha^2 = 1 - \beta^2$ (through port)

Port 4 : Ideally , no power is transmitted (isolated port)

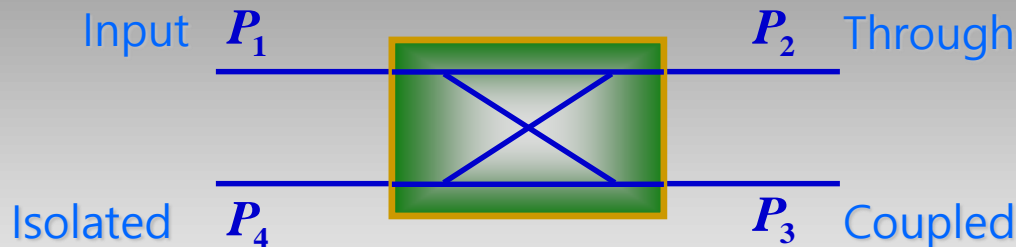Definition of Terms relevant to Directional coupler



$$\text{Coupling} = C = 10 \log \frac{P_1}{P_3} = 10 \log \frac{1}{\beta^2} = -20 \log \beta \quad (\text{dB})$$

$$\begin{aligned} \text{Directivity} = D &= 10 \log \frac{P_3}{P_4} = 10 \log \frac{P_3}{P_1} \frac{P_1}{P_4} = 10 \log \frac{\beta^2}{|S_{14}|^2} \\ &= 20 \log \frac{\beta}{|S_{14}|} \quad (\text{dB}) \end{aligned}$$

$$\text{Isolation} = I = 10 \log \frac{P_1}{P_4} = -20 \log |S_{14}| \quad (\text{dB})$$

$$(I = D + C \quad (\text{dB}))$$

Eg.①) For a Coupling factor of 3 dB ($\alpha = \beta = 1/\sqrt{2}$) and a phase Difference of 90° between port 2 and port 3, we have

⇒ quadrature hybrid

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix} \Rightarrow [S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

Eg.②) For a Coupling factor of 3 dB ($\alpha = \beta = 1/\sqrt{2}$) and phase difference of 180° between ports 4 and 1, we have

⇒ magic-T or rat-race hybrid

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix} \Rightarrow [S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

7.2 T-junction Power Divider

Lossless Divider

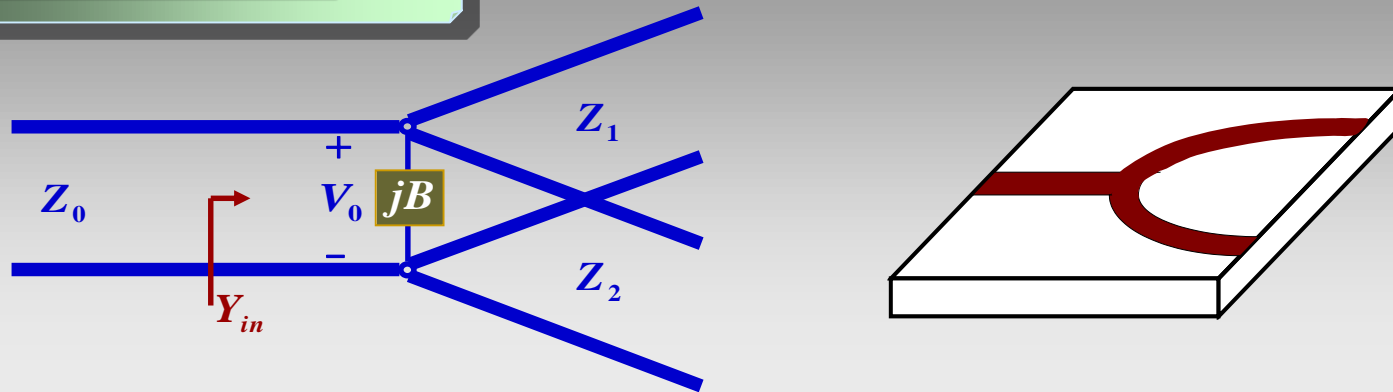


Fig. 7.6 Transmission line model of a lossless T-junction


Match condition
$$Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

B : stored energy at the junction discontinuity

Z_1, Z_2 Enable the setting of power distribution ratio

VII- 16

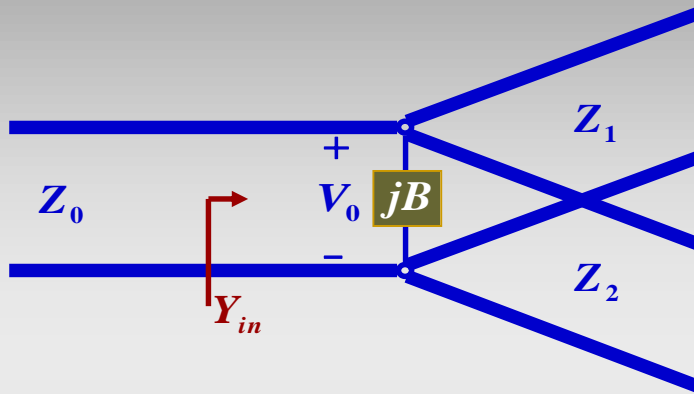Eg. 7.1) For T-junction power divider of $Z_0 = 50 \Omega$, determine Z_1, Z_2 for P_{in} divided in the ratio 1 : 2). Assume $B = 0$



$$P_{in} = \frac{1}{2} \frac{V_0^2}{Z_0}$$

$$\text{from } P_1 = \frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} P_{in} ,$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} P_{in}$$

$$Z_1 = 3Z_0 = 150 \Omega , Z_2 = \frac{3}{2} Z_0 = 75 \Omega$$

$$Z_{in} = 75 // 150 = 50 \Omega \text{ Which matches with } Z_0$$

looking from 150Ω line

$$Z_{in} = 50 // 75 = 30 \Omega$$

Looking from 75Ω line

$$Z_{in} = 50 // 150 = 37.5 \Omega$$

There is no matching, looking from the output port

7.3 Wilkinson Power Divider

- Lossy 3-port network with match at all ports
- When only Output ports are matched, we have lossless operation
- Reflected power dissipated in $2Z_0$ resistor and not delivered to other output port. i.e. $S_{32} = S_{23} = 0$. (\therefore isolation between Output ports)


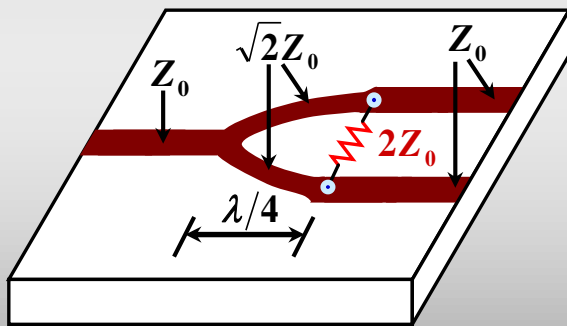


Fig. 7.8 Wilkinson power divider
(a) Microstrip form

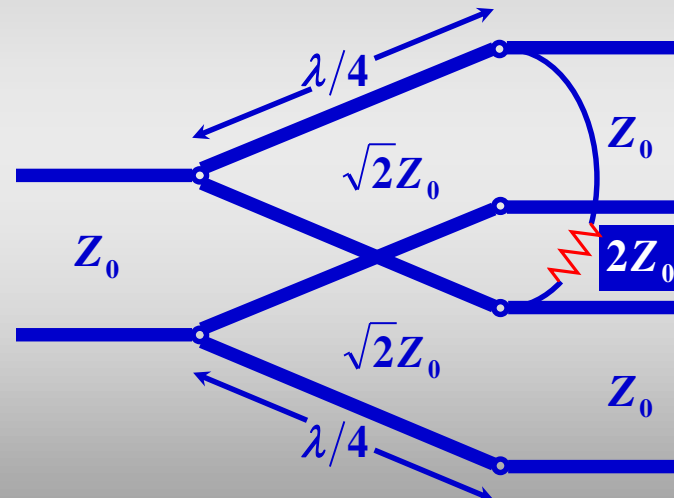

(b) Equivalent transmission line circuit

The S parameters of Wilkinson divider are

$$S_{11} = 0 \quad (Z_{in} = 1 \text{ at port 1})$$

$$S_{22} = S_{33} = 0 \quad (\text{port 2 and 3 matched for even and odd modes})$$

$$S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = \frac{-j\sqrt{2}V + 0}{V + V} = \frac{-j\sqrt{2}V}{2V} = -\frac{j}{\sqrt{2}}$$

(symmetry due to reciprocity)

$$S_{13} = S_{31} = -\frac{j}{\sqrt{2}} \quad (\text{symmetry of ports 2 and 3})$$

$$S_{23} = S_{32} = 0 \quad (\text{due to short or open at bisection})$$

7.5 Quadrature (90°) Hybrid

3 dB directional coupler with 90° phase difference between Output port

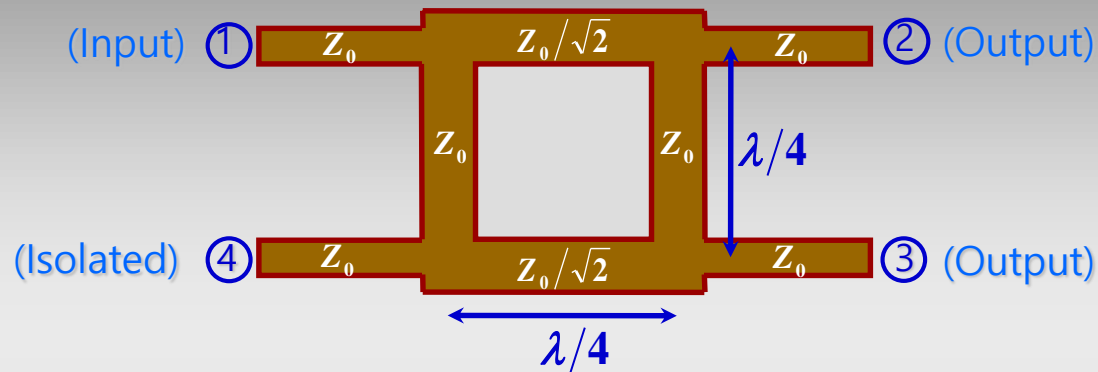



Fig. 7.21 Geometry of a branch-line coupler

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$


- All port matched
- Input at Port 1, equal division between port 2 and port 3 with 90° phase difference
- Port 4 is isolated.
- Always symmetric, irrespective of the input.

VII- 34

Design of Coupled Line Coupler

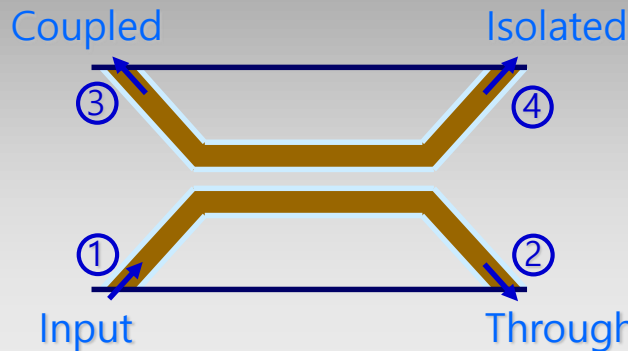


(a) Geometry and port designations

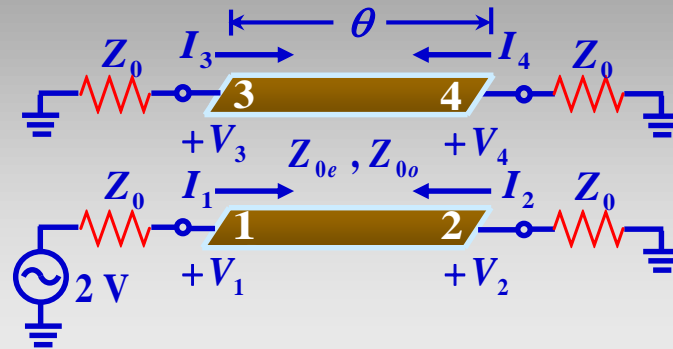

(b) The schematic circuit

Fig. 7.31 A single-section coupled line coupler

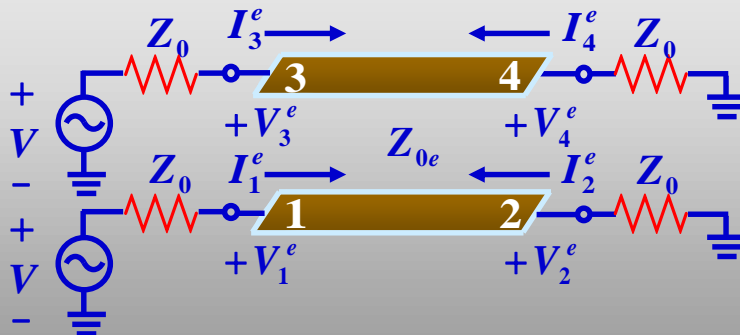

$$I_1^e = I_3^e \quad , \quad I_4^e = I_2^e$$

$$V_1^e = V_3^e \quad , \quad V_4^e = V_2^e$$

Fig. 7.32 (a) Decomposition of the coupled line coupler circuit of Fig. 7.31 into even mode

7.8 180° Hybrid

4-port network with 180° phase difference between the output ports


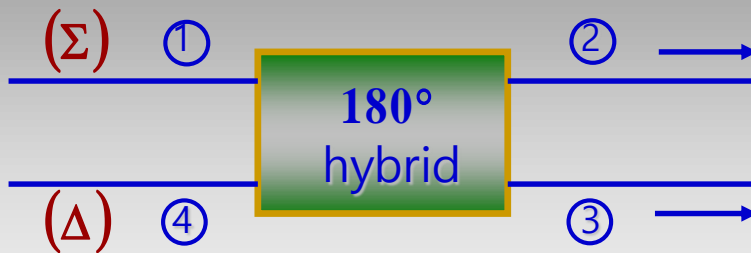



Fig. 7.41 Symbol for a 180° hybrid

$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

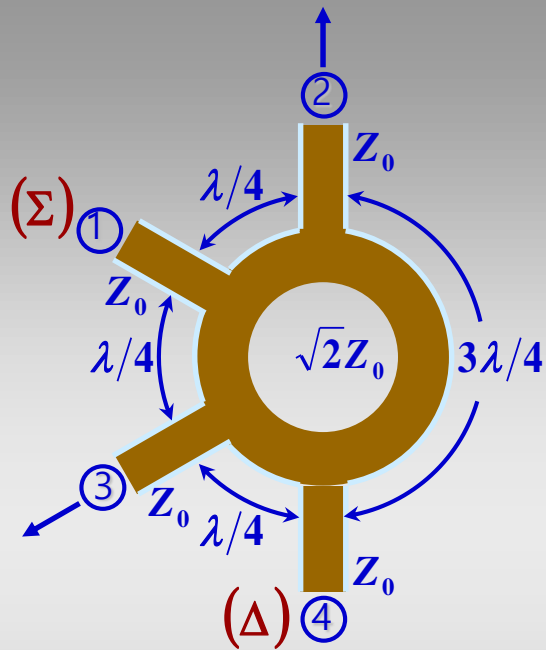
- With input at port 1, inphase output divided into ports 2 and 3, port 4 is isolated
- With input at port 4, 180° phase difference output divided into ports 2 and 3, port 1 is isolated.
- When operating as a combiner, with inputs at ports 2 and 3, sum of inputs appear at port 1 and difference of input at port 4



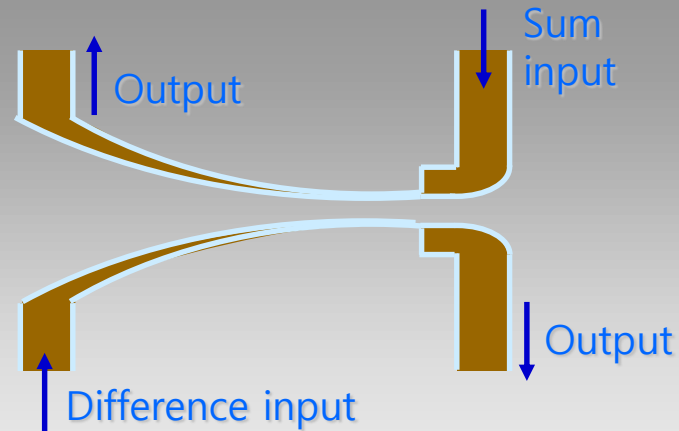(a) A ring hybrid (rat-race) in microstrip or stripline form



(b) A tapered coupled line hybrid

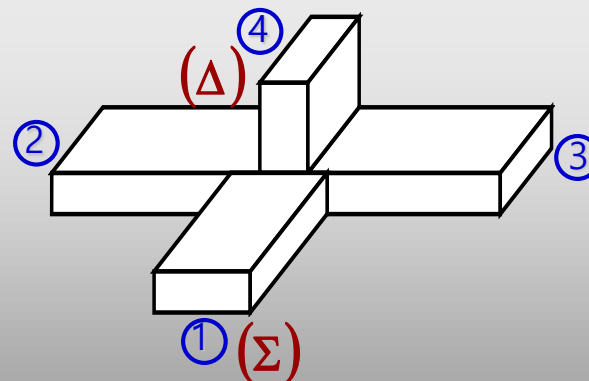

(c) A waveguide hybrid junction (magic-T)

Fig. 7.43 Hybrid junctions