

TE 364
LECTURE 5

Resonant Circuits

2018.02.25

Abdul-Rahman Ahmed

Introduction

□ **Resonant circuits** are used in many applications such as



- ❖ Filters
- ❖ Oscillators
- ❖ Tuners
- ❖ tuned amplifiers
- ❖ and microwave communication networks.

Resonant Circuits

- Near resonance,
 - ❖ RF and microwave resonant circuits
- can be represented either as
 - ❖ a lumped element series or
 - ❖ parallel RLC networks.

Series Resonant Circuits

Series Resonant Circuit

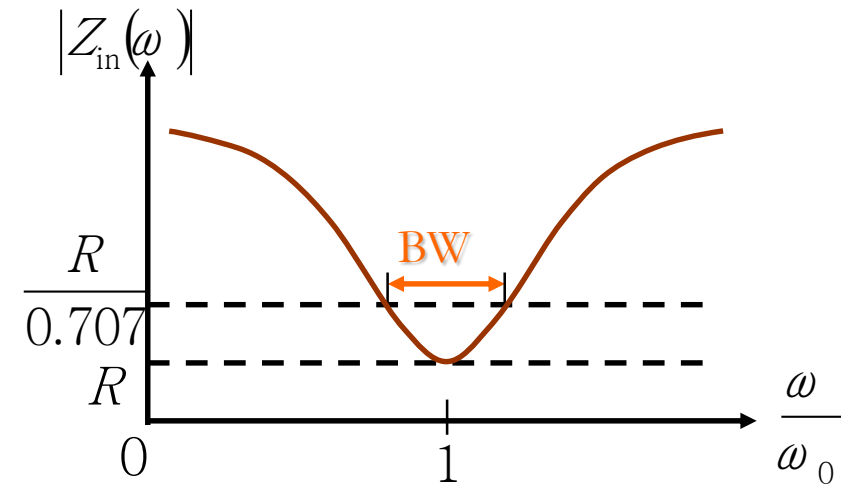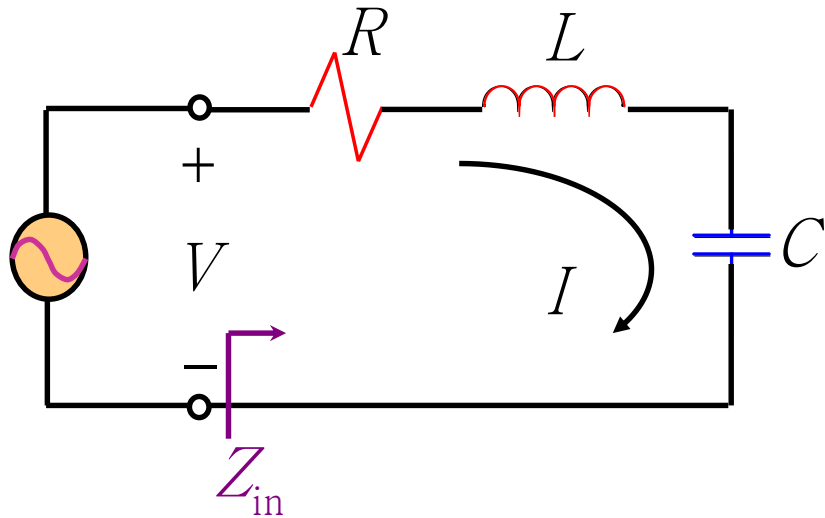

$$Z_{in} = R + j\omega L - j\frac{1}{\omega C}$$

Series Resonant Circuits

$$\begin{aligned} P_{\text{in}} &= \frac{1}{2} VI^* = \frac{1}{2} Z_{\text{in}} I I^* = \frac{1}{2} Z_{\text{in}} |I|^2 = \frac{1}{2} V \left(\frac{V}{Z_{\text{in}}} \right)^* = \frac{1}{2} \frac{|V|^2}{Z_{\text{in}}} \\ &= \frac{1}{2} |I|^2 \left(R + j\omega L - j \frac{1}{\omega C} \right) \end{aligned} \quad (6.2)$$

P_{loss} = Power dissipated by the resistor

$$P_{\text{loss}} = \frac{1}{2} |I|^2 R$$

W_m = Average magnetic energy stored in

$$W_m = \frac{1}{4} |I|^2 L$$

W_e = Average electric energy stored in

C

$$W_e = \frac{1}{4} |V_C|^2 C = \frac{1}{4} \left| \frac{I}{j\omega C} \right|^2 C = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C} \quad \left(\because v_c = \frac{1}{C} \int i dt \quad V_C = \frac{I}{j\omega C} \right)$$

Series Resonant Circuits



$$P_{in} = P_{loss} + j2\omega (W_m - W_e) \quad (6.5)$$

$$Z_{in} = \frac{2P_{in}}{|I|^2} = \frac{P_{loss} + j2\omega (W_m - W_e)}{|I|^2/2}$$


At resonance,

$$W_m = W_e$$

$$\therefore Z_{in} = \frac{P_{loss}}{|I|^2/2} = R \quad (\text{purely real})$$

$$W_m = \frac{1}{4} |I|^2 L = W_e = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C}$$


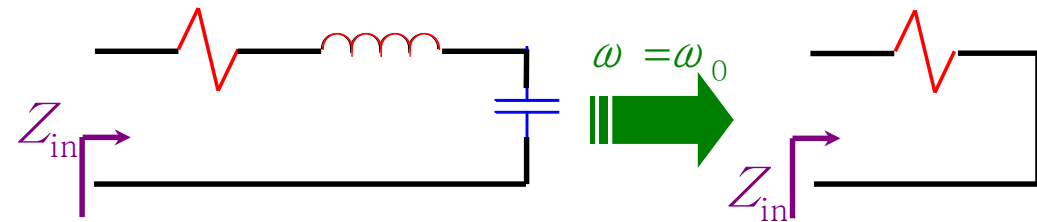
$$\omega = \frac{1}{\sqrt{LC}} = \omega_0 : \text{resonant frequency}$$



$$P_{in} = \frac{1}{2} |I|^2 R$$

Nea resonance, $Z_{in} = j2I\Delta \omega = j2I(\omega - \omega_0)$

Series Resonant Circuits

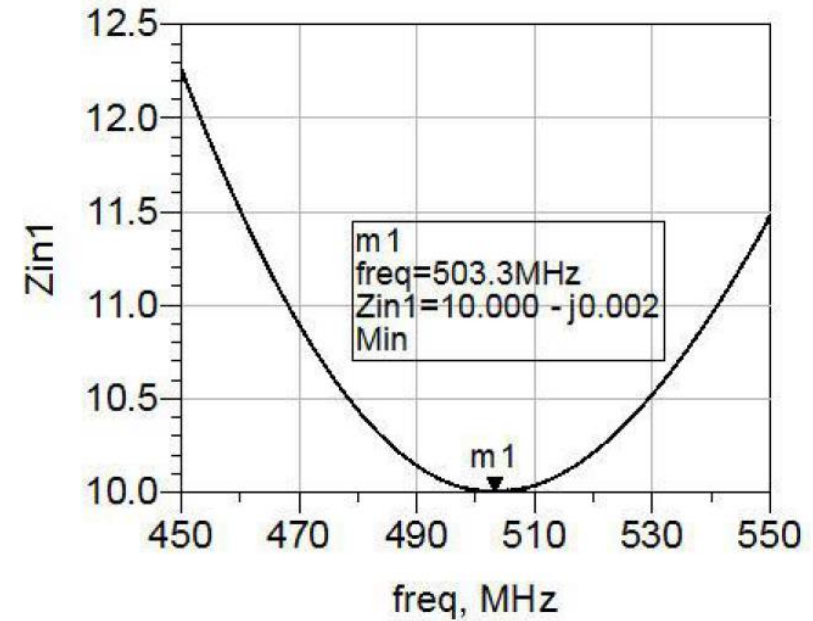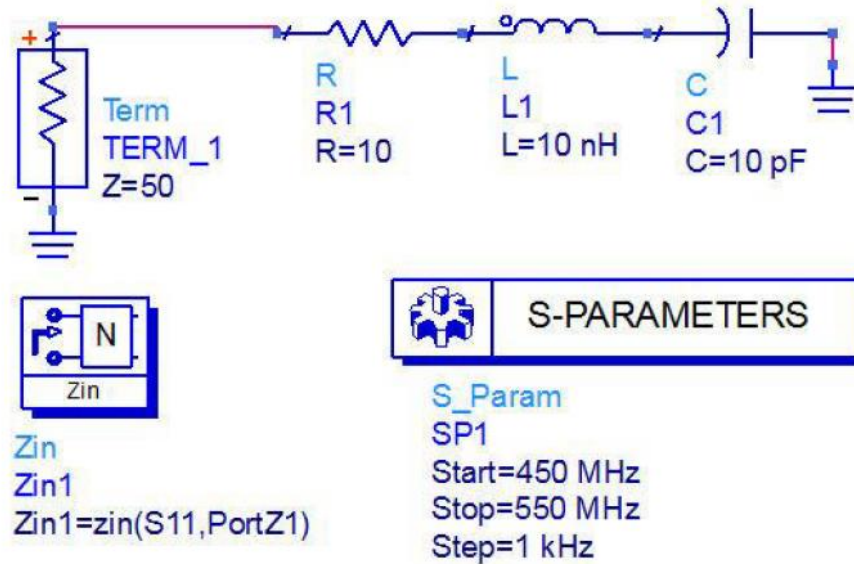

Series Resonant Circuits



Q (quality factor)

Quality Factor, Q of the series resonator is

$$Q = \omega \frac{(\text{average energy stored})}{(\text{energy loss/second})} = \omega \frac{W_m + W_e}{P_\ell}$$

At resonance, $W_m = W_e$



$$\therefore Q = \omega_0 \frac{2W_m}{P_\ell} = \omega_0 \frac{2 \frac{1}{4} |I|^2 L}{\frac{1}{2} |I|^2 R} = \frac{\omega_0 L}{R} \left(= \frac{1}{\omega_0 RC} \right) \left(\because \omega_0 = \frac{1}{\sqrt{LC}} \right)$$

❖ As R decreases, Q increases


Parallel Resonant Circuits



Parallel Resonant Circuit

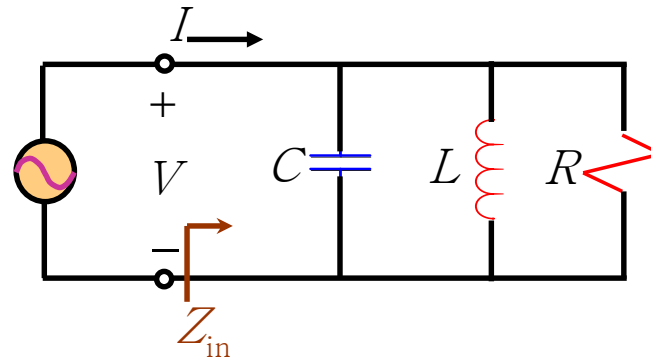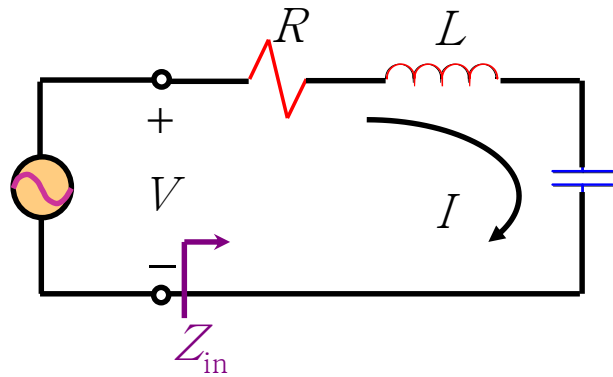
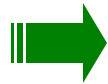
$$Z_{in} = R + j\omega L - j\frac{1}{\omega C}$$




$$Y_{in} = G + j\omega C - j\frac{1}{\omega L}$$

$$Q = \frac{\omega_0 L}{R}$$



$$Q = \frac{\omega_0 C}{G}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

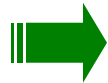


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Parallel Resonant Circuits



$$BW = \frac{1}{Q}$$


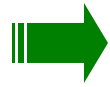


$$BW = \frac{1}{Q}$$

$$Z_{in} \approx R + j2L\Delta\omega \quad (6.9)$$


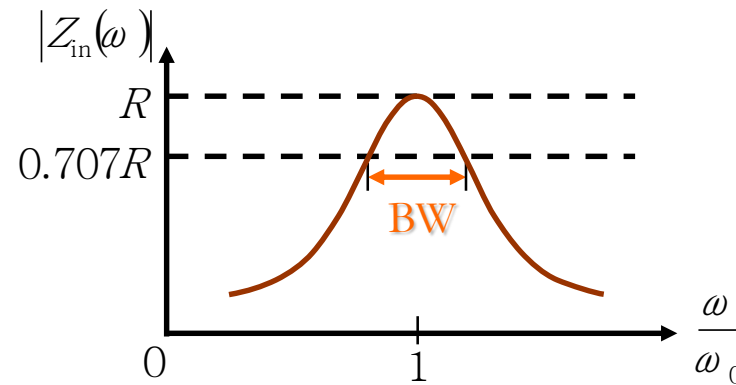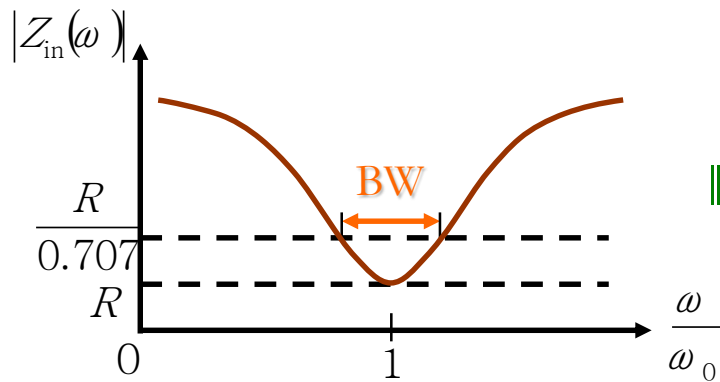
$$Y_{in} \approx G + j2C\Delta\omega \quad (6.19)$$



Parallel Resonant Circuits



- If the AC voltage across the parallel resonant circuit is V ,
 - ❖ then the complex power delivered to the resonator is

$$P_{in} = \frac{|V|^2}{2} Y_{in} = \frac{|V|^2}{2} \left(\frac{1}{R} + j\omega C - \frac{1}{j\omega L} \right)$$

- At resonance
 - ❖ power dissipated in the resistor is

$$P_{in} = \frac{|V|^2}{2R}, \quad \omega_o = \frac{1}{\sqrt{LC}}$$


Parallel Resonant Circuits

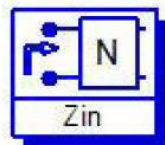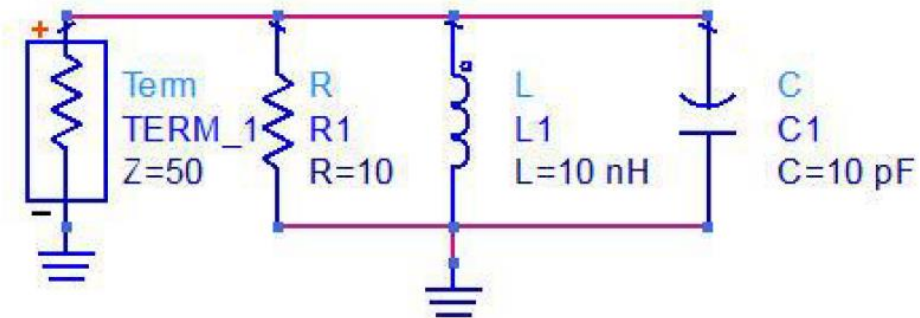

Zin
Zin1
Zin1=zin(S11,PortZ1)



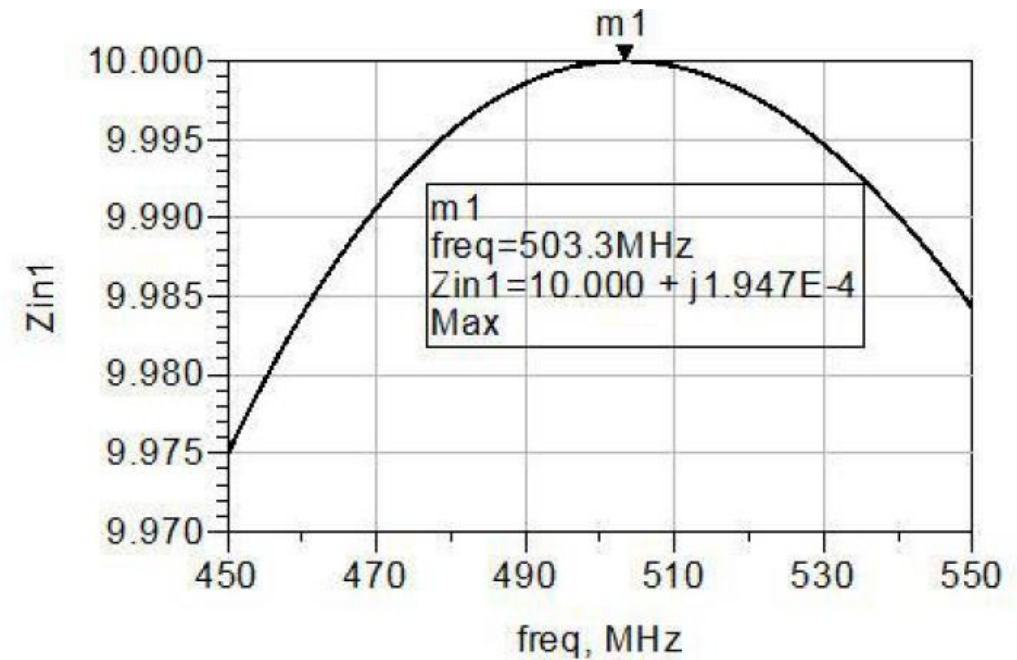S_Param
SP1
Start=450 MHz
Stop=550 MHz
Step=1 kHz



Resonant Circuit Loss

- In the resonant circuits seen so far,
 - ❖ the resistor R_1 represents the loss in the resonator.
- It includes the losses in
 - ❖ the capacitor as well as
 - ❖ the inductor.
- The Q -factor is
 - ❖ the ratio of the energy stored in the inductor and capacitor to
 - ❖ the power dissipated in the resistor as a function of frequency

Resonant Circuit Loss

- For the series resonant circuit,
 - ❖ the unloaded Q -factor is defined by:

$$Q_u = \frac{X}{R} = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR}$$

- The unloaded Q -factor of the parallel resonant circuit is simply
 - ❖ the inverse of the unloaded Q factor of the series resonant circuit.

$$Q_u = \frac{R}{X} = \frac{R}{\omega_o L} = \omega_o CR$$

Resonant Circuit Loss

□ We can clearly see that

- ❖ as the resistance increases in the series resonant circuit,
- ❖ the Q -factor decreases.

□ Conversely,

- ❖ as the resistance increases in the parallel resonant circuit,
- ❖ the Q -factor increases.


□ The Q -factor is a measure of loss in the resonant circuit. Thus

- ❖ a higher Q corresponds to lower loss and
- ❖ a lower Q corresponds to a higher loss.

Resonant Circuit Loss

Loaded Q and External Q (Q_L and Q_E)

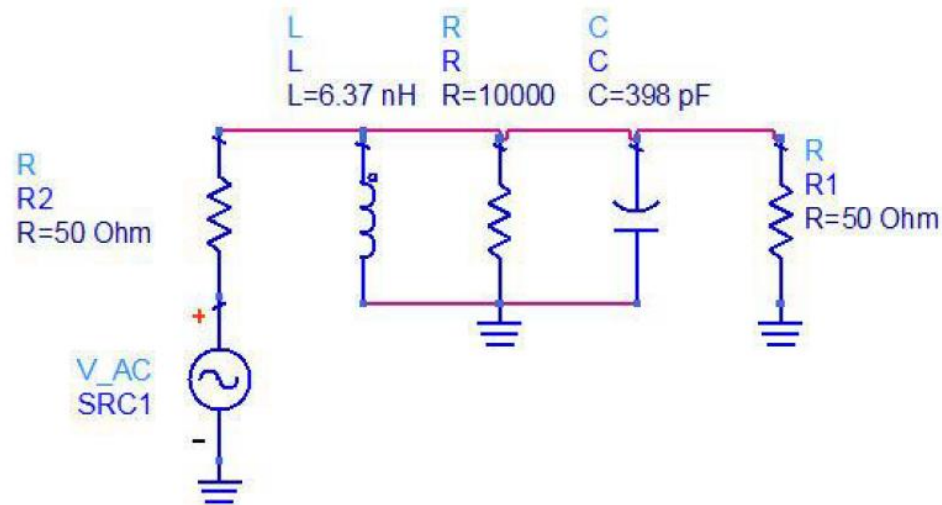- For the parallel resonator that is attached to a 50Ω source and load as shown below



$$Q_L = \frac{R_S + R + R_L}{\omega_o L}$$

$$Q_E = \frac{R_S + R_L}{\omega_o L}$$

Resonant Circuit Loss

□ The three Q -factors are related by the inverse relationship of equation

$$\frac{1}{Q_L} = \frac{1}{Q_u} + \frac{1}{Q_E}$$

□ The loaded Q is also related to the fractional bandwidth as

$$Q_L = \frac{\sqrt{f_l f_h}}{BW_{-3dB}}$$

➤ BW is the -3dB bandwidth,



➤ f_l and f_h are the lower and upper frequencies in Hz at -3dB points.

Resonant Circuit Loss

□ Example

- Design a lumped element parallel resonator at a frequency of 100 MHz. The resonator is intended to operate between a source resistance of 100Ω and a load resistance of 400Ω . use the ADS inductor and capacitor models that include the component Q factor ($L=6.37$ nH, $Q=150$; $C=398$ pF, $Q=400$).

Resonant Circuit Loss

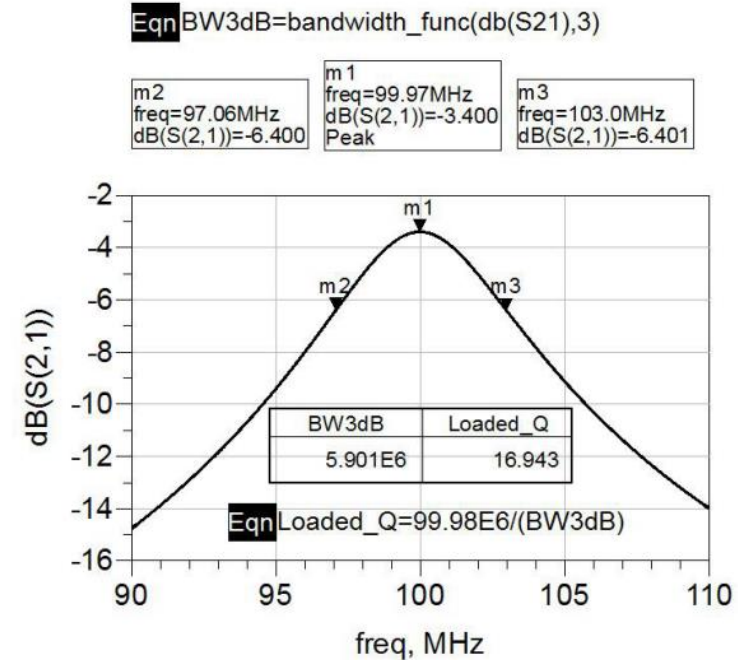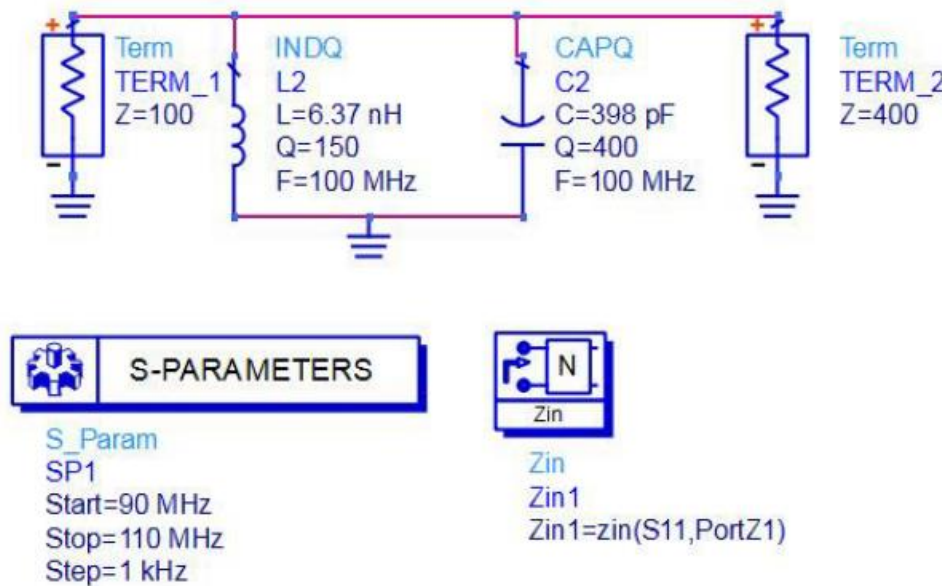

The loaded Q can be calculated from

$$Q_L = \frac{\sqrt{f_l f_h}}{BW_{-3dB}} = \frac{99.98 \text{ MHz}}{5.901 \text{ MHz}} = 16.4$$

Resonant Circuit Loss

Effect of Load Resistance on BW and Q_L

- In RF circuits and systems
 - ❖ the impedances encountered are often quite low,
 - ❖ ranging from 1Ω to 50Ω .
 - ❖ It may not be practical to have a source impedance of 100Ω and a load impedance of 400Ω .
- Lower resistances such as 50Ω will
 - ❖ Lower the bandwidth and thus
 - ❖ Lower the loaded Q

Resonant Circuit Loss

Effect of Load Resistance on BW and Q_L

- To maintain the high Q of the resonator when attached to a load such as 50Ω ,
 - ❖ it is necessary to transform the low impedance to high impedance presented to the load.
 - ❖ The 50Ω impedance can be transformed to the higher impedance of the parallel resonator thereby
 - resulting in less loading of the resonator impedance.
 - ❖ This is referred to as loosely coupling the resonator to the load.

Resonant Circuit Loss

- The tapped-capacitor and tapped-inductor networks
 - ❖ can be used to accomplish this Q transformation in lumped element circuits.

- Replacing the capacitor in the parallel network with a tapped capacitor,

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$R_{L1} = R_L \left(1 + \frac{C_1}{C_2} \right)^2$$

- R_{L1} is the higher transformed load resistance (required for the high Q)
- R_L is the desired termination impedance, say 50Ω
- C_T is simply the original capacitance and C_1 and C_2 results from tapping

Resonant Circuit Loss

□ A tapped inductor can also be used to the same effect at the source

$$R_{S1} = R_S \left(\frac{L_T}{L_1} \right)^2$$

$$L_T = L_1 + L_2$$

Practical Microwave Resonators

- At higher RF and microwave frequencies
 - ❖ small values of inductance and capacitance are physically unrealizable.
 - ❖ So resonators are seldom realized with discrete lumped element RLC components.
 - ❖ Even if the values could be physically realized the resulting Q factors would be unacceptably low for most applications.

Practical Microwave Resonators

- At higher RF and microwave frequencies
 - ❖ Resonators can be realized in all of the basic transmission line forms
 - ❖ There are many specialized resonators such as
 - ceramic dielectric resonator pucks that are coupled to a microstrip transmission line as well as
 - Yittrium Iron Garnet spheres that are loop coupled to its load.
 - ❖ These resonators are optimized for very high Q factors
 - ❖ and may be tunable over a range of frequencies.

Resonant Circuit Loss

Home Work

- ❖ In the parallel LC Example, change the load from 400Ω to 50Ω and re-examine the circuit's 3 dB bandwidth and Q_L .
- ❖ Rearrange the parallel LC network with the tapped capacitor network and Re-examine the circuit's 3 dB bandwidth and Q_L .
- ❖ Do same for the inductor and re-examine the circuit's 3 dB bandwidth and Q_L .