

# TE 364

## LECTURE 6

# Filter Circuits

2018.02.25

Abdul-Rahman Ahmed

---

# Outline

---

## □ Basic Filters and Terminology

- ❖ Low-pass, High-pass, band-pass and band-stop

## □ Passive Filters Synthesis

- ❖ Image Parameter Method
- ❖ Insertion Loss Method

## □ Microwave Filters

# Introduction





## □ A Filter

- ❖ is a two-port network
- ❖ used to control the frequency response at a certain point in an RF or microwave system
- ❖ by providing **transmission** at frequencies within the passband of the filter and
- ❖ **attenuation** in the stopband of the filter.

# Basic Filter Types


- 
- Typical frequency responses include:
    - ❖ low-pass,
    - ❖ high-pass,
    - ❖ bandpass, and
    - ❖ band-reject characteristics.

# Basic Filter Types

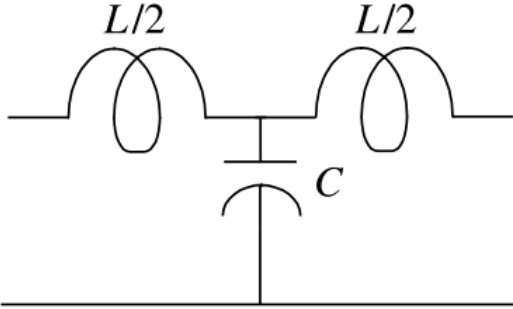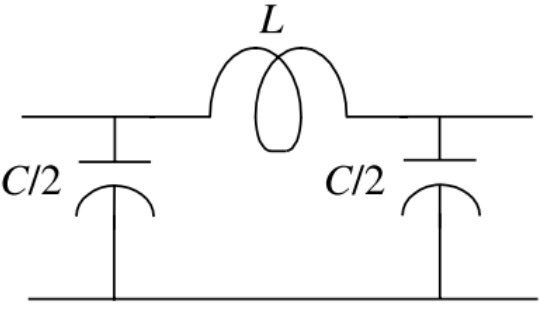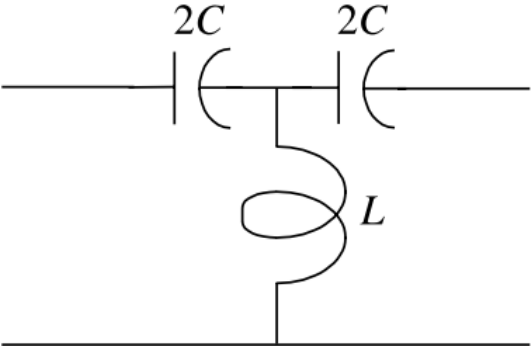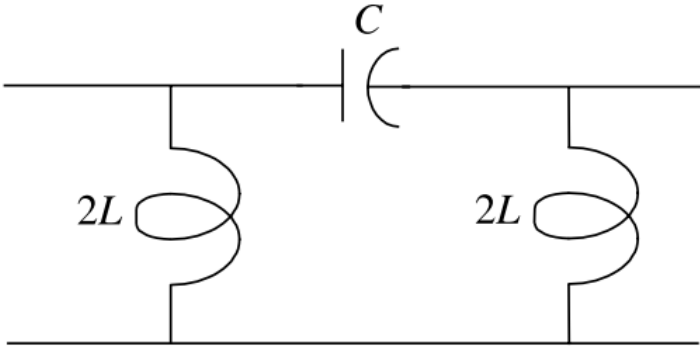
Filter Type	T-Section	$\pi$ -Section
Low-pass		
High-pass		

# Basic Filter Types



## Band-pass

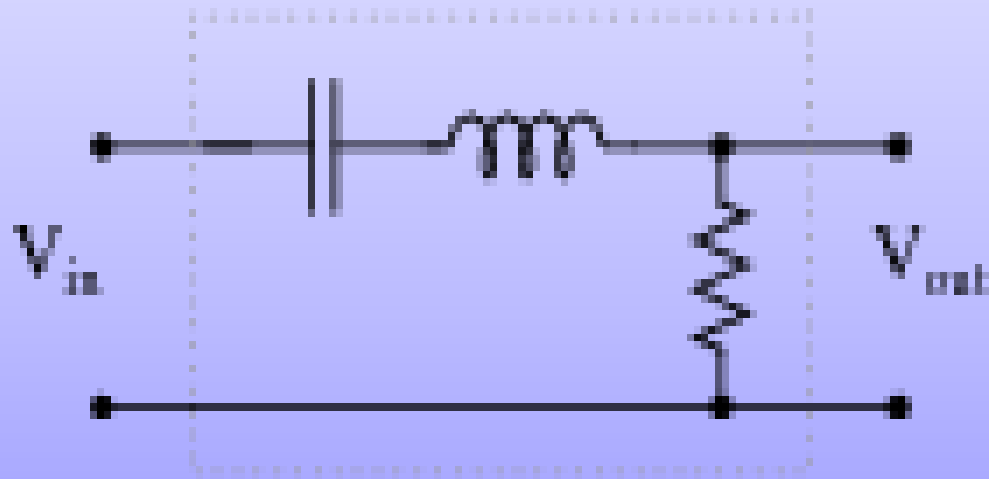



## Band-stop

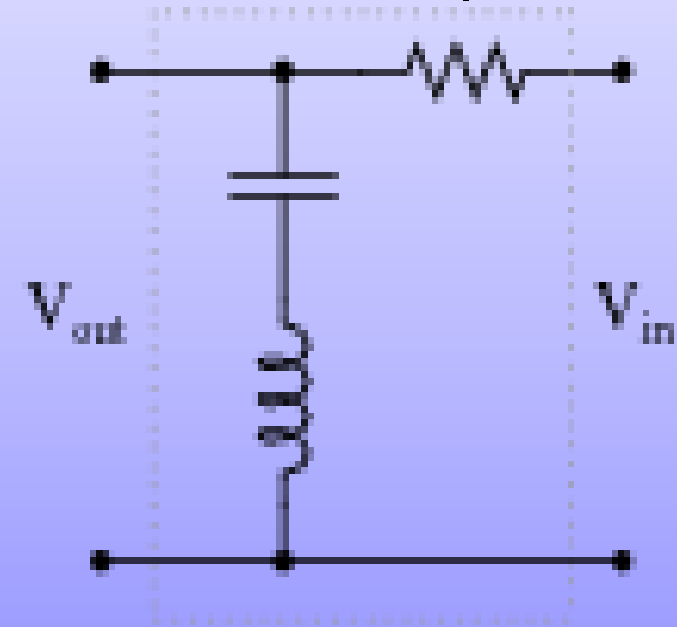

# Filter Frequency Response

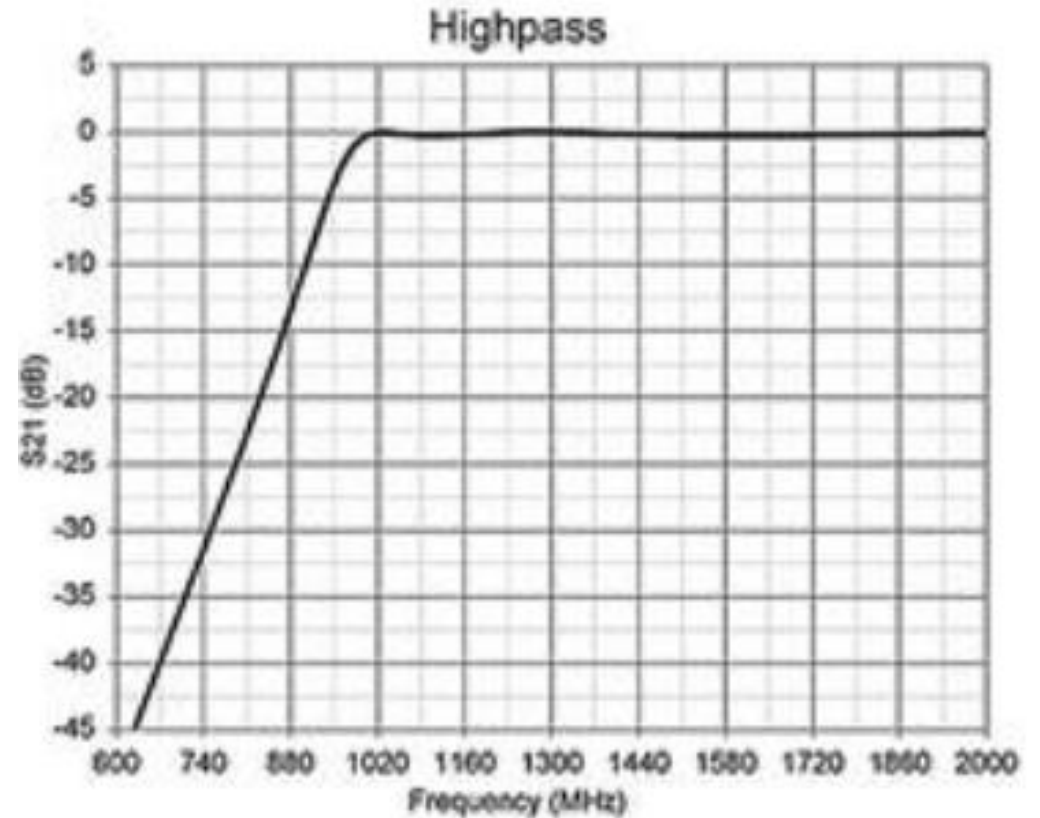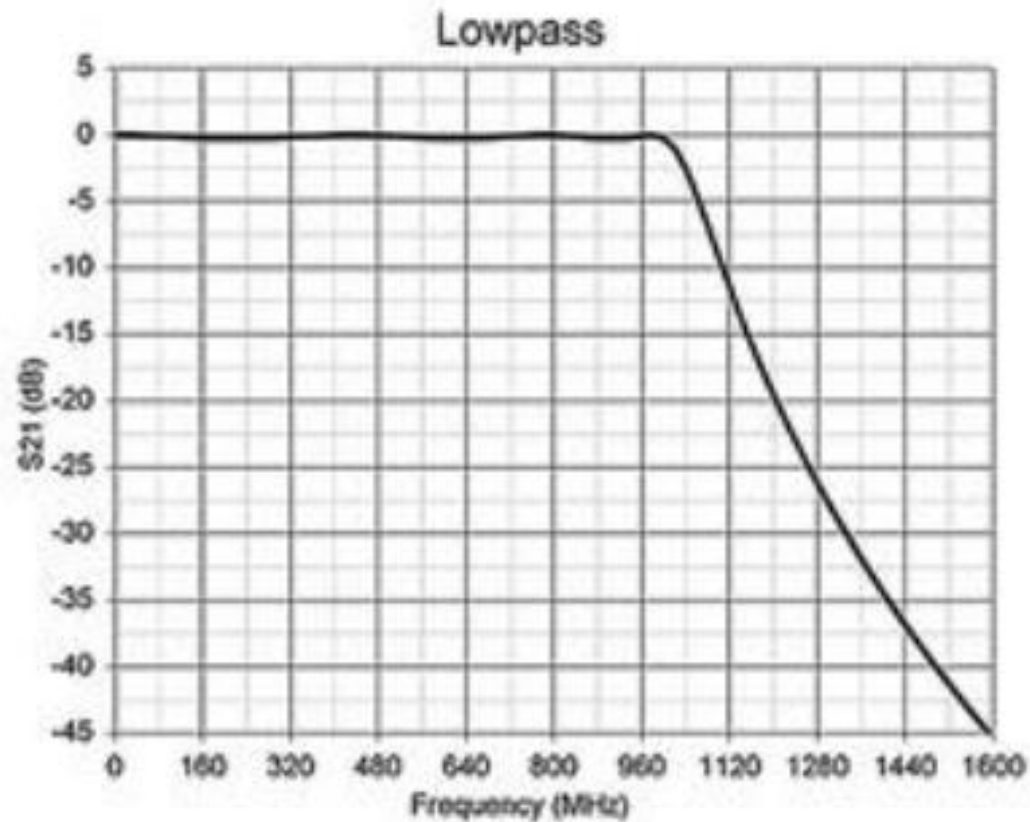

# Filter Frequency Response

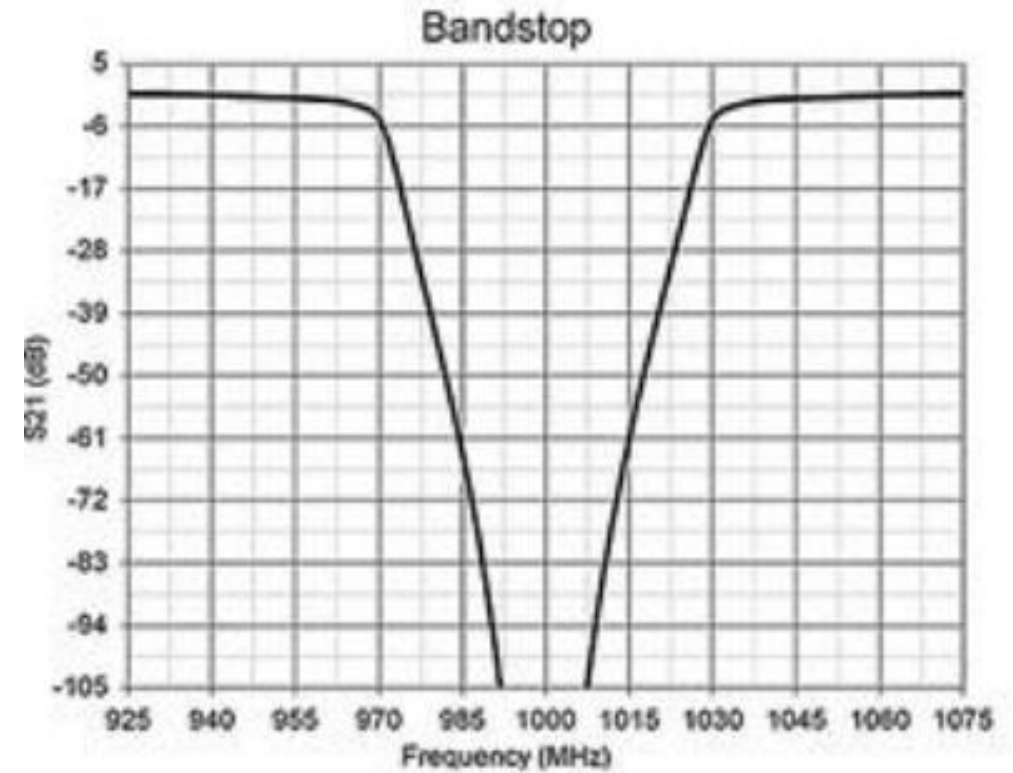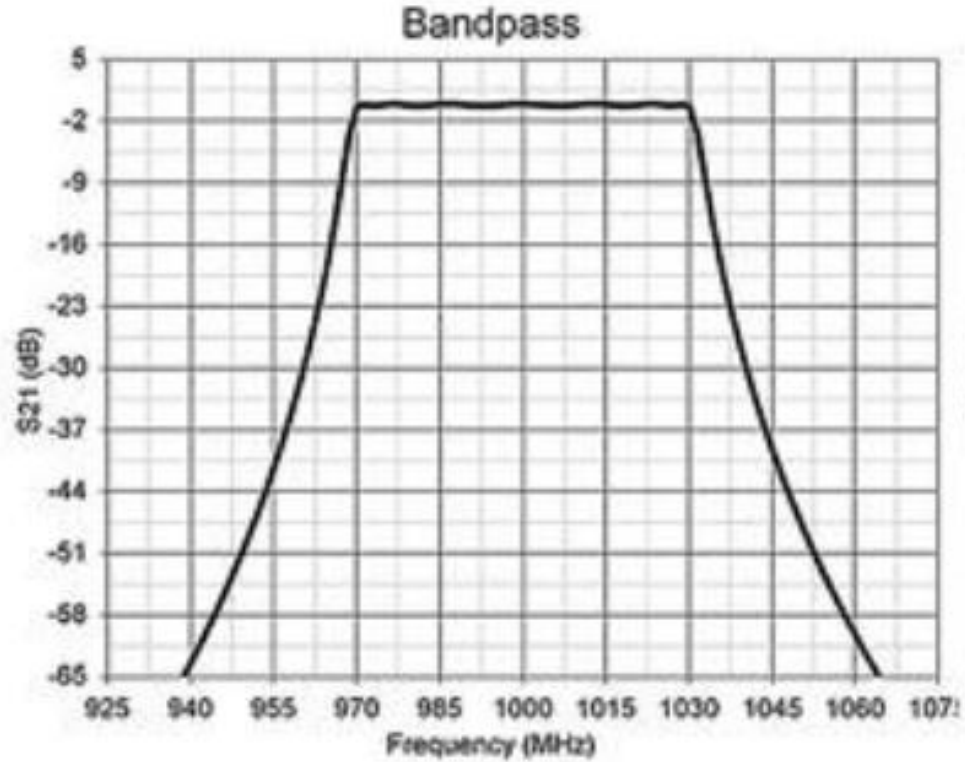



# Important Terminologies

## □ Insertion Loss (in dB)

- ❖ The ratio of the power delivered by a source to a load with and without a two-port network inserted in between.

## □ Return Loss (in dB)

- ❖ The fraction of the input power that is lost due to reflection at its input port

## □ Attenuation (in dB or Nepers)

- ❖ The ratio of the power delivered to a matched load to that supplied to it by a matched source

# Filter Classification

---

## □ Active filters

- ❖ can amplify the signal besides blocking the undesired frequencies

## □ Passive filters

- ❖ are economical and easy to design.
- ❖ perform fairly well at higher frequencies

# Filter Design Methods

## □ *Image parameter method*


- ❖ provides a design that can pass or stop a certain frequency band but
- ❖ its frequency response cannot be shaped.

## □ *Insertion-loss method*

- ❖ Is more powerful in the sense that
- ❖ it provides a specified response of the filter.

# Image Parameter Method

□ Consider the two-port network

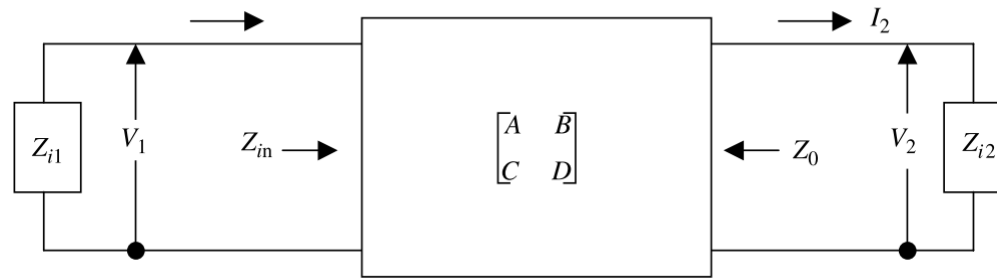

❖  $Z_{i1}$  and  $Z_{i2}$  are the image impedance of the network

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{AV_2 + BI_2}{CV_2 + DI_2} = \frac{AZ_{i2} + B}{CZ_{i2} + D}$$

# Image Parameter Method

□ It can be shown that

$$\begin{aligned}V_2 &= DV_1 - BI_1 \\ I_2 &= -CV_1 + AI_1\end{aligned}$$

$$Z_o = -\frac{V_2}{I_2} = -\frac{DV_1 - BI_1}{-CV_1 + AI_1} = \frac{DZ_{i1} + B}{CZ_{i1} + A}$$

❖ *Note that*

$$Z_{i1} = -\frac{V_1}{I_1}$$

# Image Parameter Method

□ It can further be shown that;

❖ For  $Z_{i1} = Z_{in}$  and  $Z_{i2} = Z_o$

$$Z_{i1} = \sqrt{\frac{AB}{CD}}$$

❖ and

$$Z_{i2} = \sqrt{\frac{BD}{AC}}$$

# Image Parameter Method

□ Furthermore;

❖ The transfer characteristics is given by

$$\frac{V_1}{V_2} = A + B \frac{I_2}{V_2} = A + \frac{B}{Z_{i2}}$$

❖ or

$$\frac{V_1}{V_2} = \sqrt{\frac{A}{D}} (\sqrt{AD} + \sqrt{BC})$$

# Image Parameter Method

□ Or

$$\frac{V_2}{V_1} = \sqrt{\frac{D}{A}} (\sqrt{AD} - \sqrt{BC})$$

❖ Note that,  $AD - BC = 1$  for reciprocal networks

□ Similarly



$$\frac{I_2}{I_1} = \sqrt{\frac{A}{D}} (\sqrt{AD} - \sqrt{BC})$$



$A/D$  is X'former ratio  
taken as 1 in this case

❖ And  $e^{-\gamma} = \sqrt{AD} - \sqrt{BC}$  or  $\cosh \gamma = \sqrt{AD}$







# Image Parameter Method

## ❖ Parameters for T and Pi-networks

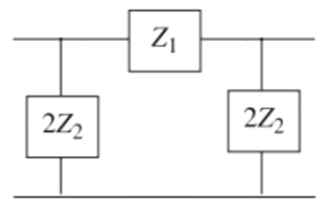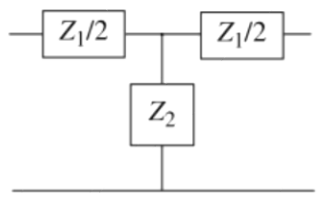	$\pi$ -Network	T-Network
		
<i>ABCD</i> parameters	$A = 1 + \frac{Z_1}{2Z_2}$ $B = Z_1$ $C = \frac{1}{Z_2} + \frac{Z_1}{4Z_2^2}$ $D = 1 + \frac{Z_1}{2Z_2}$	$A = 1 + \frac{Z_1}{2Z_2}$ $B = Z_1 + \frac{Z_1^2}{4Z_2}$ $C = \frac{1}{Z_2}$ $D = 1 + \frac{Z_1}{2Z_2}$
Image impedance	$Z_{i\pi} = \sqrt{\frac{Z_1 Z_2}{1 + Z_1/4Z_2}} = \frac{Z_1 Z_2}{Z_{iT}}$	$Z_{iT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$
Propagation constant, $\gamma$	$\cosh \gamma = 1 + \frac{Z_1}{2Z_2}$	$\cosh \gamma = 1 + \frac{Z_1}{2Z_2}$

# Image Parameter Method

## ❖ Constant $k$ -filter sections

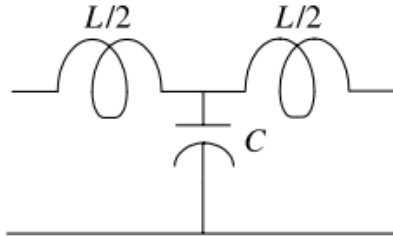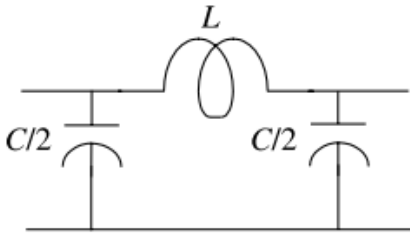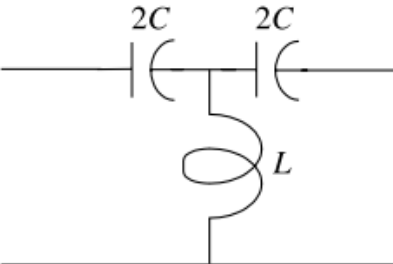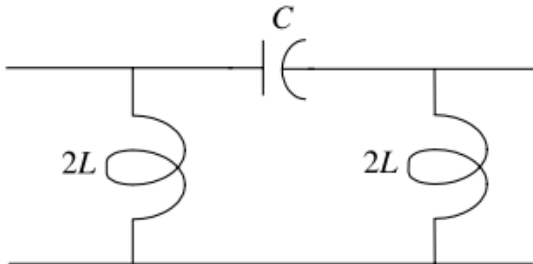Filter Type	T-Section	$\pi$ -Section
Low-pass		
High-pass		

# Image Parameter Method

□ For the low-pass T-section,

$$Z_1 = j\omega L \quad Z_2 = \frac{1}{j\omega C}$$

❖ Therefore, the image impedance from Table is

$$Z_{iT} = \sqrt{\frac{L}{C} \left( 1 - \frac{\omega^2 LC}{4} \right)}$$

❖ In the case of D.C.

$$Z_{iT} = \sqrt{\frac{L}{C}} \quad (\text{Nominal Impedance})$$

# Image Parameter Method

❖ For  $Z_{iT}$  to be equal to 0, (*Cut-off frequency,  $\omega_c$* )

❖ 
$$\frac{\omega^2 LC}{4} = 1 \quad \longrightarrow \quad \omega_c = \frac{2}{\sqrt{LC}}$$

# Image Parameter Method

□ For the high-pass T-section,

$$Z_1 = \frac{1}{j\omega C} \quad Z_2 = j\omega L$$

❖ Therefore, the image impedance from Table is

$$Z_{iT} = \sqrt{\frac{L}{C} \left( 1 - \frac{1}{4\omega^2 LC} \right)}$$

❖ The cut-off frequency is

$$\omega_c = \frac{1}{2\sqrt{LC}}$$

# Image Parameter Method

## ❖ *Example*


➤ Design a low-pass constant-k T-section that has a nominal impedance of  $75 \Omega$  and a cut-off frequency of 2 MHz.

## ❖ *Solution*


$$Z_{iT} = 75 \Omega = \sqrt{\frac{L}{C}} \quad , \quad \omega_c = 2 \times 2\pi \times 10^6 = \frac{2}{\sqrt{LC}}$$

$$L = 11.9366 \mu\text{H} \text{ and } C = 2.122 \text{ nF}$$

# Image Parameter Method

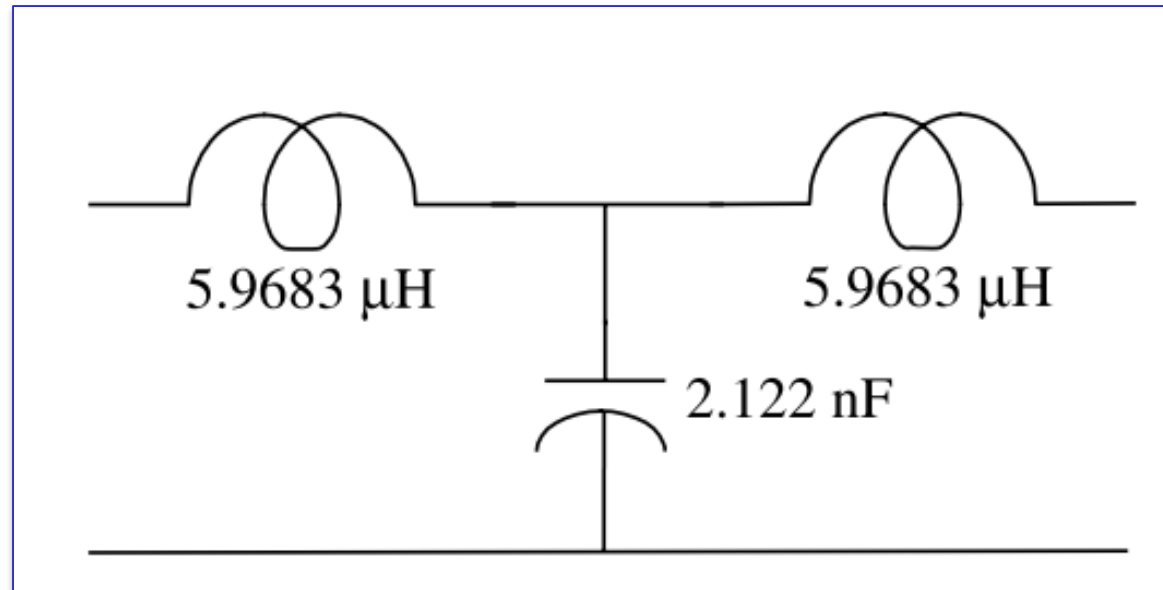


# Image Parameter Method

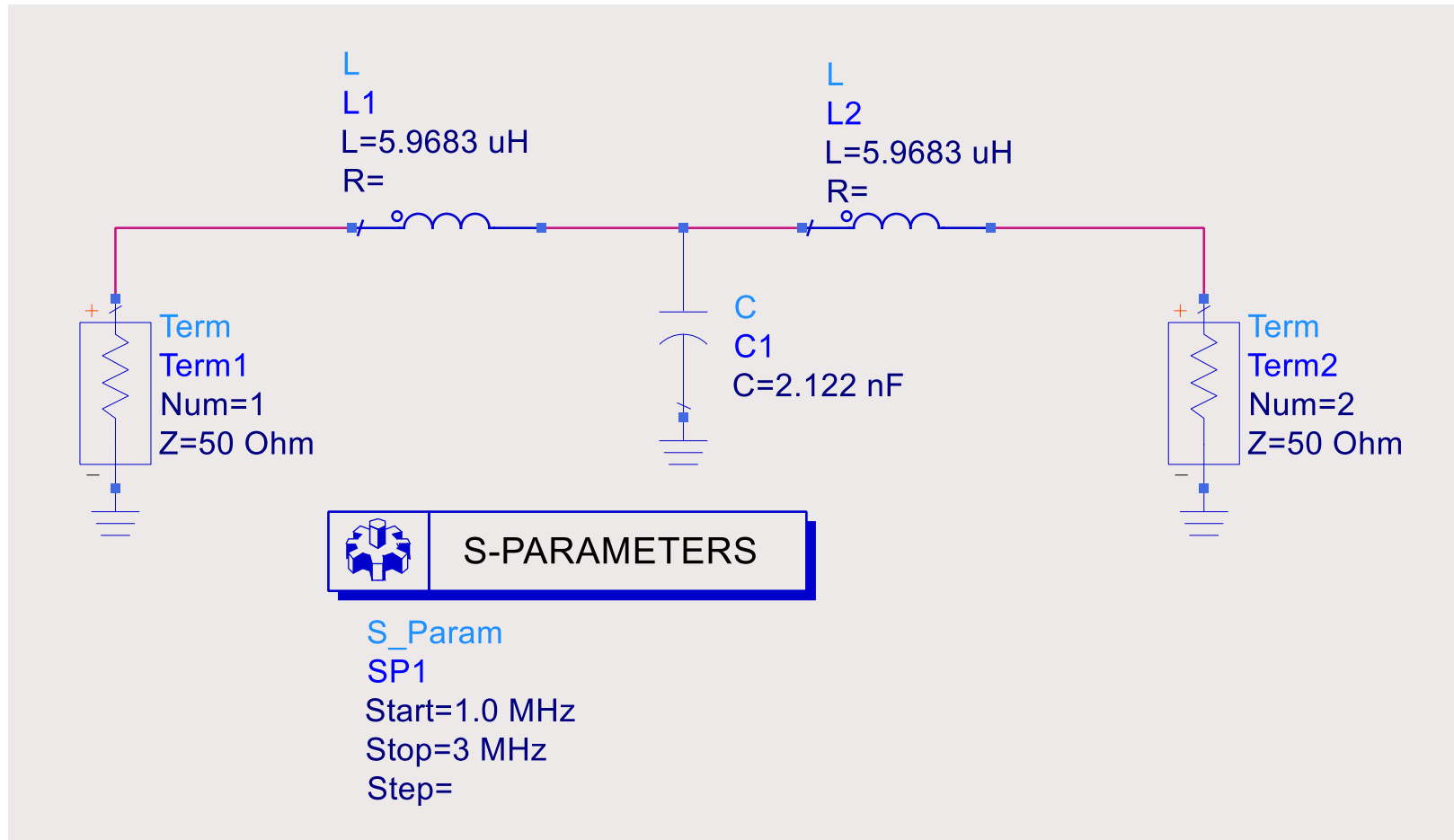



# Image Parameter Method

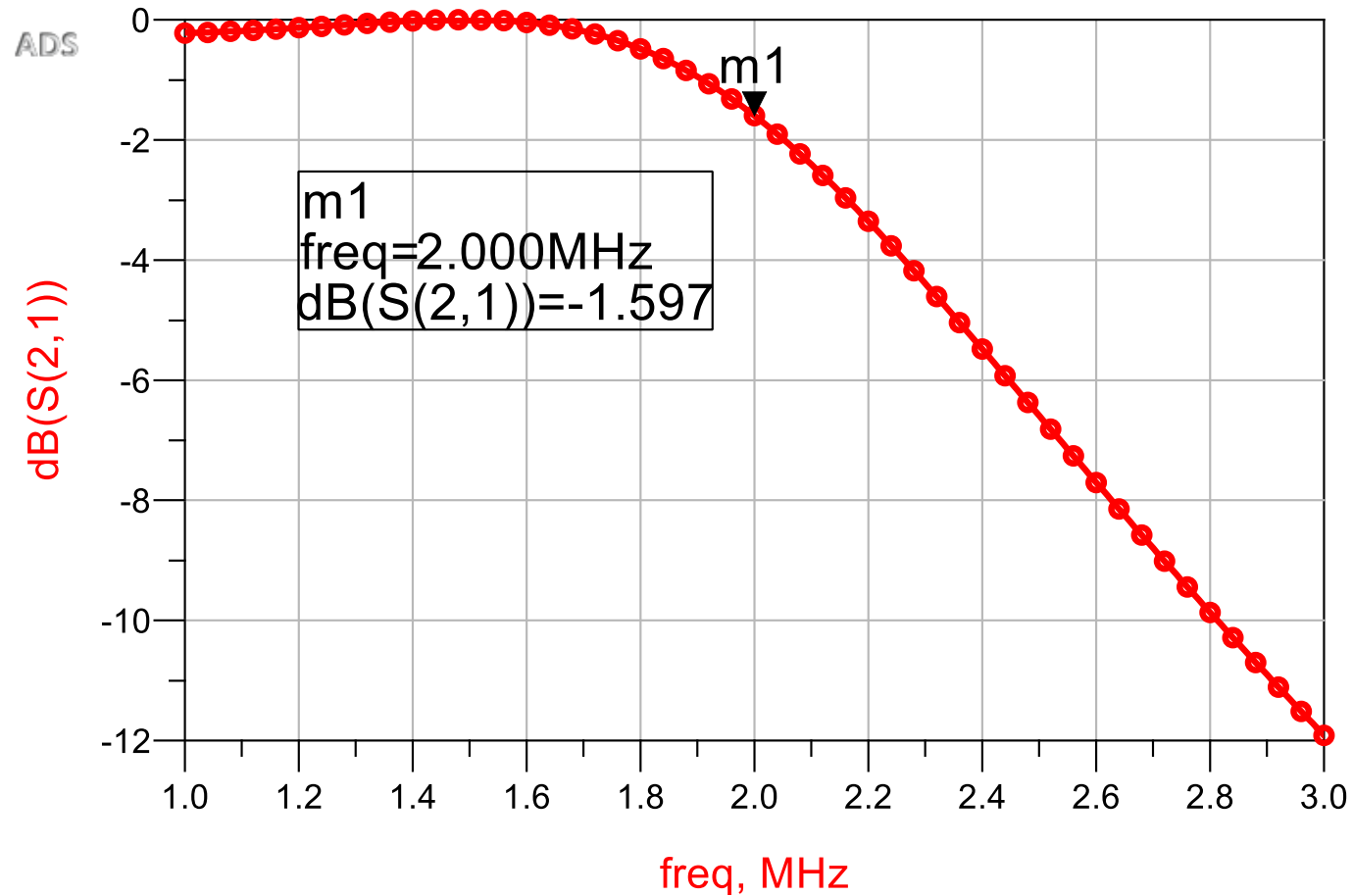

# Image Parameter Method

## ❑ Disadvantage of Image Parameter


- ❖ The signal attenuation rate after the cut-off point is not very sharp,
- ❖ The image impedance is not constant with frequency.
- ❖ From a design point of view, it is important that it is constant, at least in its pass-band.

## ❑ Solution:

- ❖ **M-derived Filter Section**

# M-Derived Filter Section

□ Consider the following two T-sections

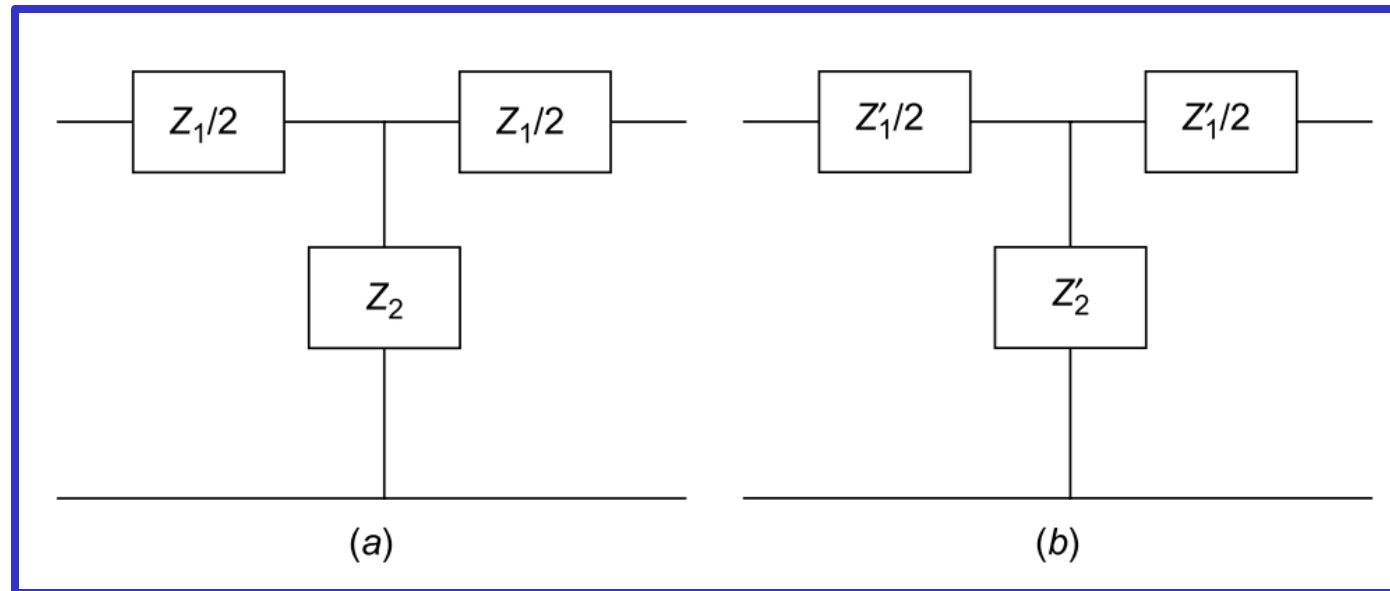

$$Z_{iT} = Z'_{iT} = \sqrt{Z'_1 Z'_2 \left( 1 + \frac{Z'_1}{4Z'_2} \right)} = \sqrt{Z_1 Z_2 \left( 1 + \frac{Z_1}{4Z_2} \right)}$$

# M-Derived Filter Section

$$Z'_2 = \frac{1}{Z'_1} \left( Z_1 Z_2 + \frac{Z_1^2 - Z_1'^2}{4} \right)$$

Let  $Z'_1 = mZ_1$

$$Z'_2 = \frac{Z_2}{m} + \frac{1 - m^2}{4m} Z_1$$

- Thus, an  $m$ -derived section is designed from the values of components determined for the corresponding constant- $k$  filter.
- The value of  $m$  is selected to sharpen the attenuation at cut-off
- or to control the image impedance characteristics in the pass-band.

# M-Derived Filter Section

□ For the low-pass T-section,

$$Z'_1 = j\omega mL \quad Z'_2 = \frac{1-m^2}{4m} j\omega L + \frac{1}{j\omega mC}$$

❖ Therefore, the transfer function is

$$\frac{Z'_1}{Z'_2} = -\frac{\omega^2 m^2 LC}{1 - \left[ \frac{(1-m^2)}{4} \right] \omega^2 LC} = \frac{4\omega^2 m^2 / \omega_c^2}{1 - (1-m^2)\omega^2 / \omega_c^2}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

# M-Derived Filter Section

□ From the table of parameters on slide 17,

$$\cosh \gamma = 1 + \frac{Z'_1}{2Z'_2} = 1 - \frac{2(m\omega/\omega_c)^2}{1 - (1 - m^2)(\omega/\omega_c)^2}$$

$$\cosh \gamma = \frac{\omega_c^2 - \omega^2 - (m\omega)^2}{\omega_c^2 - (1 - m^2)\omega^2}$$

# M-Derived Filter Section

□  $\cosh \gamma \rightarrow \infty$  if

$$\omega = \frac{\omega_c}{\sqrt{1 - m^2}} = \omega_\infty$$

□ Condition used to sharpen *attenuation cut-off*

- ❖ Small  $m$  means  $\omega \cong \omega_\infty$
- ❖  $\omega_\infty$  selected slightly higher than  $\omega_c$
- ❖  $m$  is then determined from the above condition
- ❖  $Z'_1$  and  $Z'_2$  can then be determined from equations on slide 21


# M-Derived Filter Section

- Note: image impedance of  $m$ -derived T-section
  - ❖ is same as that of corresponding constant- $k$  network
- In the case of Pi-network
  - ❖ It is a function of  $m$
- A characteristics used to design input and output network of the filter so that:
  - ❖ Image impedance of composite network stays constant in its pass band


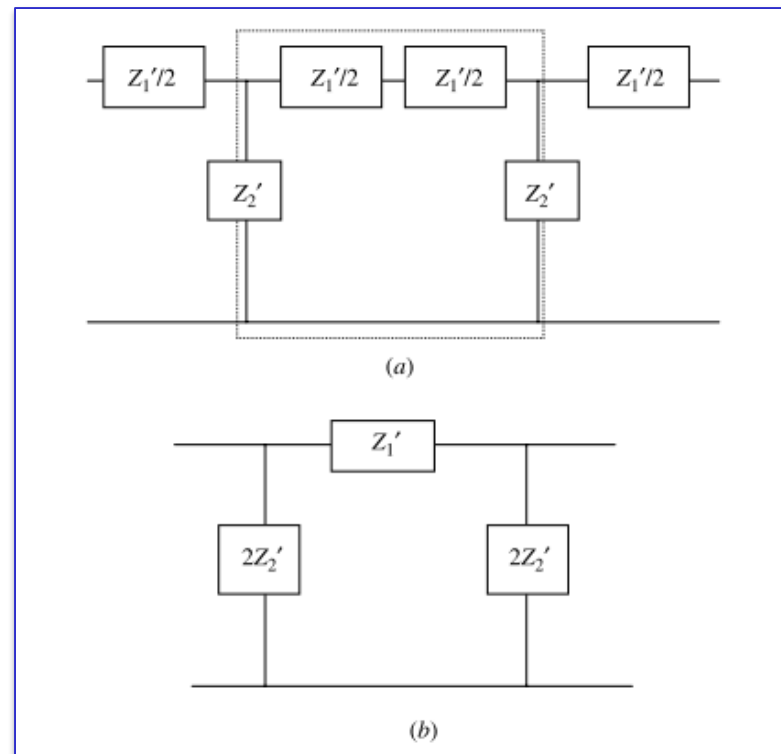
# M-Derived Filter Section

- Note: an infinite cascade of T-networks
  - ❖ Can be considered as Pi-network after splitting shunt arm.



# M-Derived Filter Section

- Note: of th  $Z'_2 \Gamma$ -network is replaced by  $2Z'_2$
- Also two halves of the series arms give  $Z'_1$
- From the table of parameters on slide 13,

$$Z_{i\pi} = \frac{Z'_1 Z'_2}{Z_{iT}} = \frac{Z_1 Z_2 + \left[ (1 - m^2) / 4 \right] Z_1^2}{Z_{iT}}$$

- For the low-pass constant k-filter

$$Z_1 Z_2 = \frac{L}{C} = Z_o^2$$

$$Z_1^2 = -\omega^2 L = -\left( \frac{2Z_o \omega}{\omega_c} \right)^2$$

# M-Derived Filter Section

and,

$$Z_{iT} = Z_0 \sqrt{1 - \left(\frac{\omega}{\omega_c}\right)^2}$$

Therefore,


$$Z_{i\pi} = \frac{1 - (1 - m^2) (\omega/\omega_c)^2}{\sqrt{1 - (\omega/\omega_c)^2}} Z_0$$

$$\text{or } \bar{Z}_{i\pi} = \frac{1 - (1 - m^2) \bar{\omega}^2}{\sqrt{1 - \bar{\omega}^2}}$$

$$\bar{Z}_{i\pi} = Z_{i\pi} / Z_0$$

$$\bar{\omega} = \omega / \omega_c$$

# M-Derived Filter Section

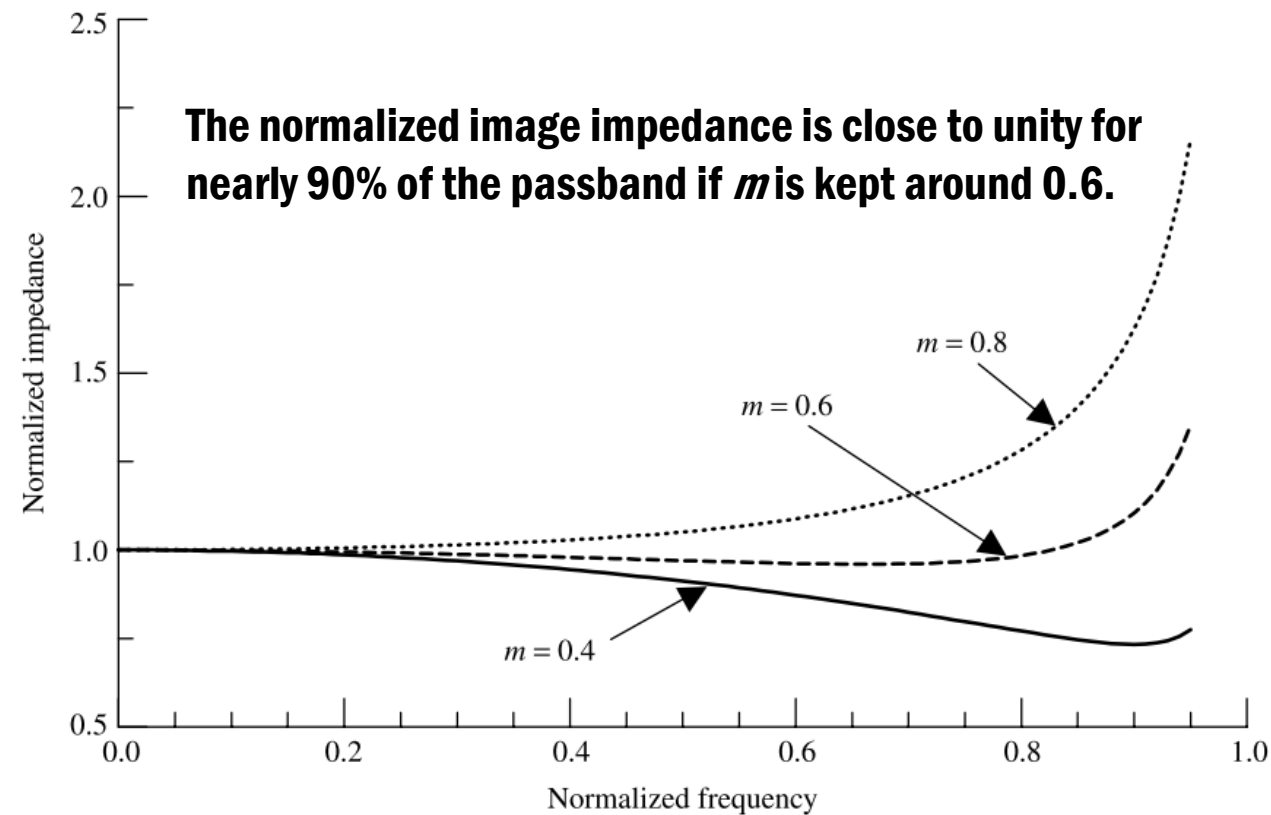

Normalized image impedance of  $\pi$  -network versus normalized frequency for three values of  $m$ .

# M-Derived Filter Section

## ❖ *Example*

- Design an  $m$ -derived T-section low pass filter with a cut-off frequency of 2 MHz and a nominal impedance of 75  $\Omega$ . The infinity frequency  $f_\infty$  is 2.05 MHz.

## ❖ *Solution*

$$Z_{iT} = 75\Omega = \sqrt{\frac{L}{C}} \quad \omega_c = 2 \times \pi \times 10^6 = \frac{2}{\sqrt{LC}}$$

$$L = 11.9366 \mu\text{H} \text{ and } C = 2.122 \text{ nF}$$

$$\omega = \frac{\omega_c}{\sqrt{1-m^2}} = \omega_\infty \Rightarrow 1-m^2 = \left(\frac{f_c}{f_\infty}\right)^2$$


# M-Derived Filter Section

$$m = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2} = \sqrt{1 - \left(\frac{2}{2.05}\right)^2} = 0.2195$$

$$mL/2 = 0.2195 \times 5.9683 = 1.31 \mu\text{H}$$

$$mC = 0.2195 \times 2.122 = 465.78 \text{ nF}$$
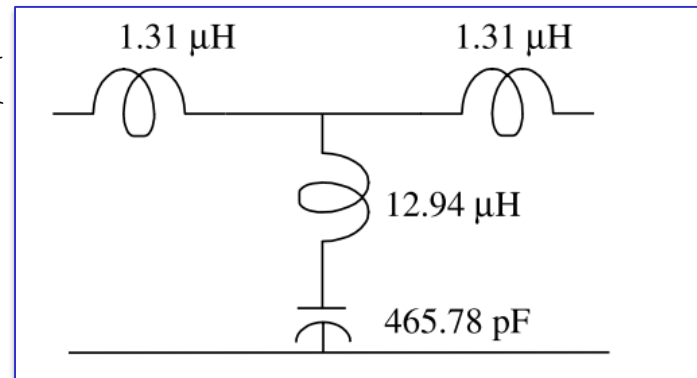
$$\frac{1 - m^2}{4m} L = 12.94 \mu\text{H}$$



# Composite Filters

- ❑  $m$ -derived filter provides sharp attenuation at cut-off
  - ❖ but attenuation in its stop-band is unacceptably low
- ❑ constant- $k$  filter shows a higher attenuation in its stop-band,
  - ❖ but the change is unacceptably gradual
- ❑ Composite Filters: cascading these two filters
  - ❖ Taking advantage of each.


# Composite Filters

- Since image impedance stays the same in two cases,
  - ❖ this cascading will not create a new impedance matching problem.
  - ❖ However image impedance varies with frequency at the input and output ports of the network.
- Input and output matching therefore required



# Composite Filters

□ Consider the bisected pi-section below

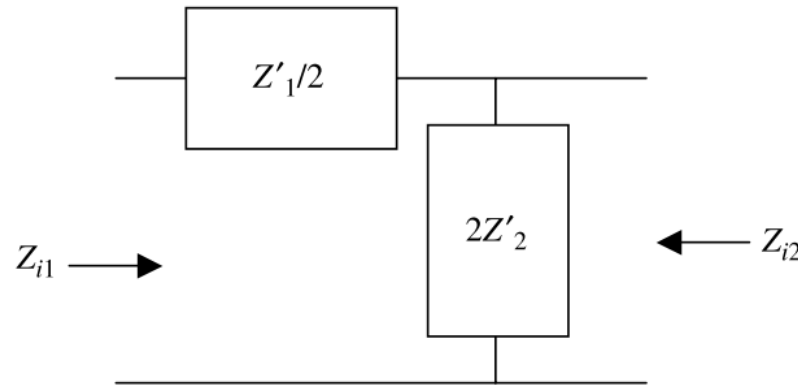

$$A = 1 + \frac{Z'_1}{4Z'_2} \quad B = \frac{Z'_1}{2} \quad C = \frac{1}{2Z'_2} \quad D = 1$$

# Composite Filters

□ The image impedances are:

$$Z_{i1} = \sqrt{Z_1'Z_2' + \frac{Z_1'^2}{4}} = Z_{iT}$$





$$Z_{i2} = \sqrt{\frac{Z_1'Z_2'}{1 + Z_1'/4Z_2'}} = \frac{Z_1'Z_2'}{Z_{iT}} = Z_{i\pi}$$

❖ the bisected  $\pi$  -section can be connected at the input and output ports of cascaded constant-k and  $m$ -deri-ved sections to obtain a composite filter that

□ solves the impedance problem.

# M-Derived Filter Section

**TABLE 9.3 Design Relations for Composite Filters**

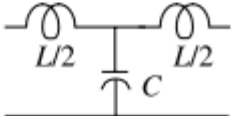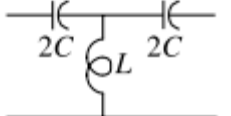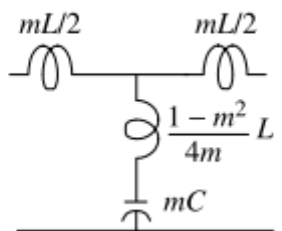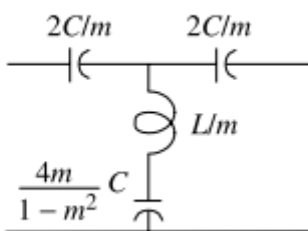
Low-Pass	High-Pass
<p><i>Constant-k T-filter</i></p>  $Z_0 = \sqrt{L/C}$ $\omega_c = 2/\sqrt{LC}$ $L = 2Z_0/\omega_c$ $C = 2/Z_0\omega_c$	<p><i>Constant-k T-filter</i></p>  $Z_0 = \sqrt{L/C}$ $\omega_c = 1/2\sqrt{LC}$ $L = 0.5Z_0/\omega_c$ $C = 0.5/Z_0\omega_c$
<p><i>m-derived T-Section</i></p> <p>(Values of <math>L</math> and <math>C</math> are the same as above)</p> $m = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2}$ 	<p><i>m-derived T-Section</i></p> <p>(Values of <math>L</math> and <math>C</math> are the same as above)</p> $m = \sqrt{1 - \left(\frac{f_\infty}{f_c}\right)^2}$ 

# Input & Output Matching Sections


Low-Pass

High Pass

*Input and Output Matching Sections*

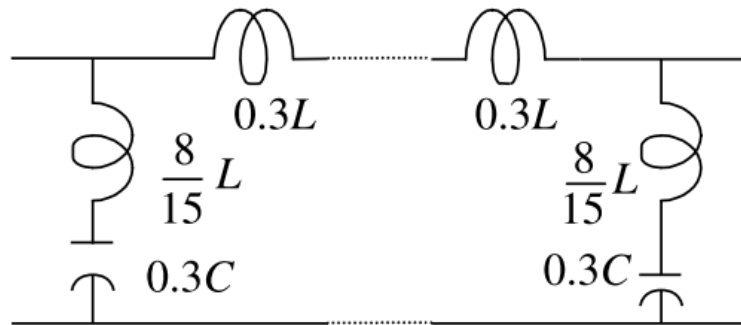

*Input and Output Matching Sections*

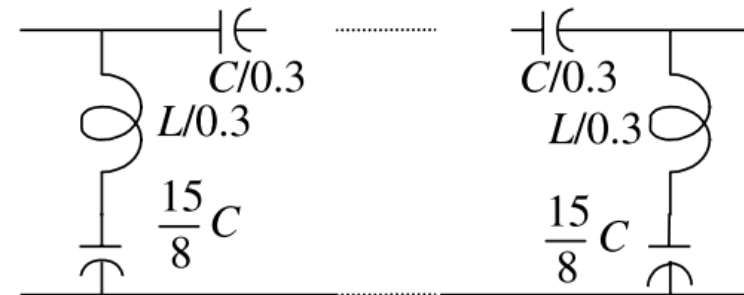

# Composite Filters

## ❖ *Example*

- Design a high-pass composite filter with a nominal impedance of  $75\Omega$ . It must pass all signals over 2 MHz. Assume that  $f_\infty = 1.95$  MHz.

## ❖ *Solution*

From Table 9.3 (slide 31), we find the components of its constant- $k$  section as follows.

$$L = \frac{75}{2 \times 2 \times \pi \times 2 \times 10^6} \text{H} = 2.984 \mu\text{H}$$

and

$$C = \frac{1}{2 \times 2 \times \pi \times 2 \times 10^6 \times 75} \text{F} = 530.5 \text{ pF}$$

# Composite Filters

Similarly, the component values for its m-derived filter section are determined as follows:

$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_c}\right)^2} = \sqrt{1 - \left(\frac{1.95}{2}\right)^2} = 0.222$$

$$\frac{2C}{m} = 4.775 \text{ nF}$$

$$\frac{L}{m} = 13.43 \text{ } \mu\text{H}$$

$$\frac{4m}{1 - m^2} C = 0.496 \text{ nF}$$

# Composite Filters

The component values for the bisected  $\pi$  -section to be used at its input and output ports are found as

$$\frac{C}{0.3} = 1.768 \text{ nF}$$

$$\frac{L}{0.3} = 9.947 \text{ } \mu\text{H}$$

$$\frac{15}{8}C = 0.9947 \text{ nF}$$

